 


# **EEE 3101: Digital Logic and Circuits**

## **Programmable Logic Devices**

**Course Teacher: Nafiz Ahmed Chisty**

**Head, Department of EEE  
Associate Professor, Department of EEE & CoE  
Faculty of Engineering  
Room# D0105, D Building  
Email: [chisty@aiub.edu](mailto:chisty@aiub.edu)  
Website: <http://engg.aiub.edu/faculties/nafiz>  
Website: [www.nachisty.com](http://www.nachisty.com)**



# Introduction

- Programmable Logic Devices (PLD)
  - It is used to implement Boolean functions of digital systems.
  - General purpose chip for implementing circuits
  - Can be customized using programmable switches
- Advantages PLDs:
  - Less board space needed
  - Fewer printed circuit board
  - Smaller Enclosure
  - Programmability
  - Re-programmability
- Custom chips: standard cells, sea of gates


 


Fig: PLD as a Black Box

# Classification of PLD

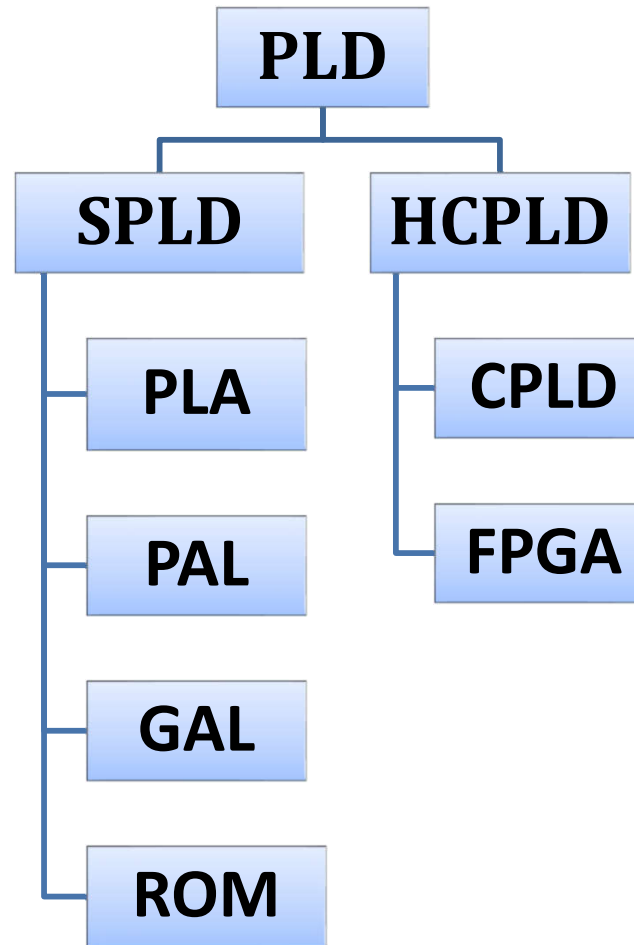

## Simple Programmable Logic Device (SPLD)

- SPLD stands for Simple Programmable Logic Device. PLA stands for Programmable Logic Array . PAL stands for Programmable Array Logic. GAL stands for Generic Array Logic.
- PAL is one time programmable (OTP). GAL is reprogrammable.
- Any SOP within a defined number of variables can be implemented using PLA, PAL and GAL.
- SPLDs must be programmed so that the switches are in the correct places
  - CAD tools are usually used to do this
    - A fuse map is created by the CAD tool and then that map is downloaded to the device via a special programming unit
  - There are two basic types of programming techniques
    - Removable sockets on a PCB
    - In system programming (ISP) on a PCB
      - This approach is not very common for PLAs and PALs but it is quite common for more complex PLDs


## ■ An SPLD Programming Unit



- The SPLD is removed from the PCB, placed into the unit and programmed there

# ■ Removable SPLD Socket Package


- PLCC (plastic-leaded chip carrier)

 


- In System Programming (ISP)
  - Used when the SPLD cannot be removed from the PCB
  - A special cable and PCB connection are required to program the SPLD from an attached computer
  - Very common approach to programming more complex PLDs like CPLDs, FPGAs, etc.

# SPLD

- PLA

 

- PAL

 




# Programmable Logic Array (PLA)


$$f_1 = x_1x_2 + x_1x_3' + x_1'x_2'x_3$$

$$f_2 = x_1x_2 + x_1'x_2'x_3 + x_1x_3$$

## Gate Level Version of PLA

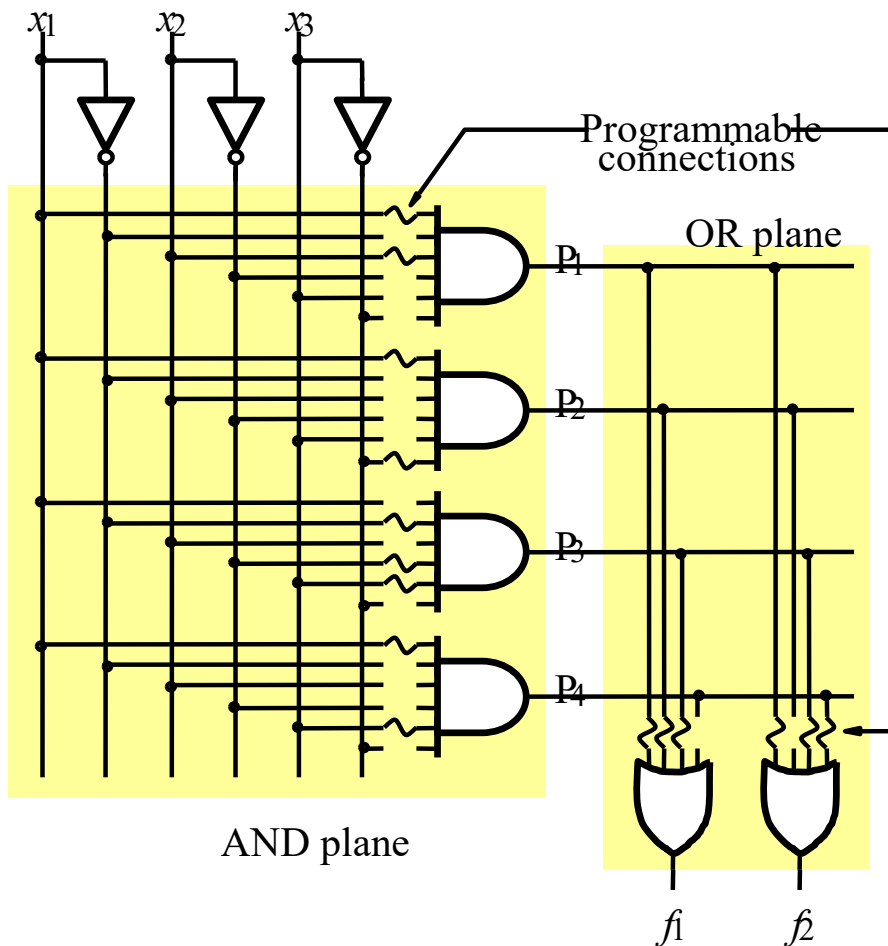

## Customary Schematic of a PLA

 



x marks the connections left in place after programming

# ■ Limitations of PLAs

- PLAs come in various sizes
  - Typical size is 16 inputs, 32 product terms, 8 outputs
    - Each AND gate has large fan-in → this limits the number of inputs that can be provided in a PLA
    - 16 inputs →  $3^{16}$  = possible input combinations; only 32 permitted (since 32 AND gates) in a typical PLA
    - 32 AND terms permitted → large fan-in for OR gates as well
      - This makes PLAs slower and slightly more expensive than some alternatives to be discussed shortly
    - 8 outputs → could have shared minterms, but not required
  
## Programmable Array Logic (PAL)

- PAL stands for Programmable Array Logic.
- It is an one time programmable device.
- PALs have many inputs and outputs.
- Each programmable link, which is a fuse incase of a PAL, is called a cell.
- Each row is connected to the input of an AND gate.
- Each column is connected to the input variable or its complement.
- By programming the presence and absence of a fuse connection, any combination of input variables or complements can be applied to AND gates.
- Only SOPs can be implemented.




## ■ Comparing PALs and PLAs


- PALs have the same limitations as PLAs (small number of allowed AND terms) plus they have a fixed OR plane → less flexibility than PLAs
- PALs are simpler to manufacture, cheaper, and faster (better performance)
- PALs also often have extra circuitry connected to the output of each OR gate
  - The OR gate plus this circuitry is called a *macrocell*
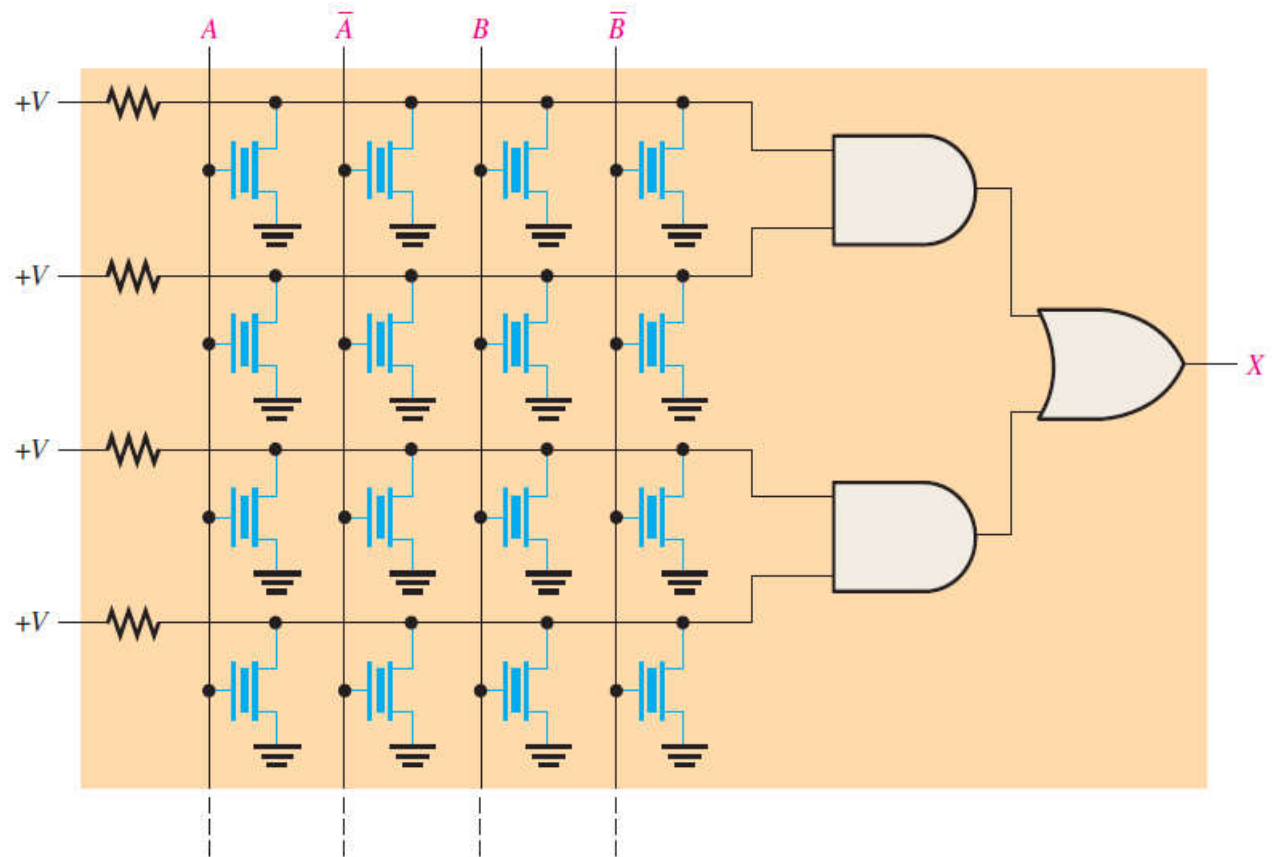
## Generic Array Logic (GAL)

- GAL works almost the same way as PAL.
- It is reprogrammable.
- Instead of fuses it uses a programmable technology such as EEPROM.




# Simplified Notation for PAL/GAL

 
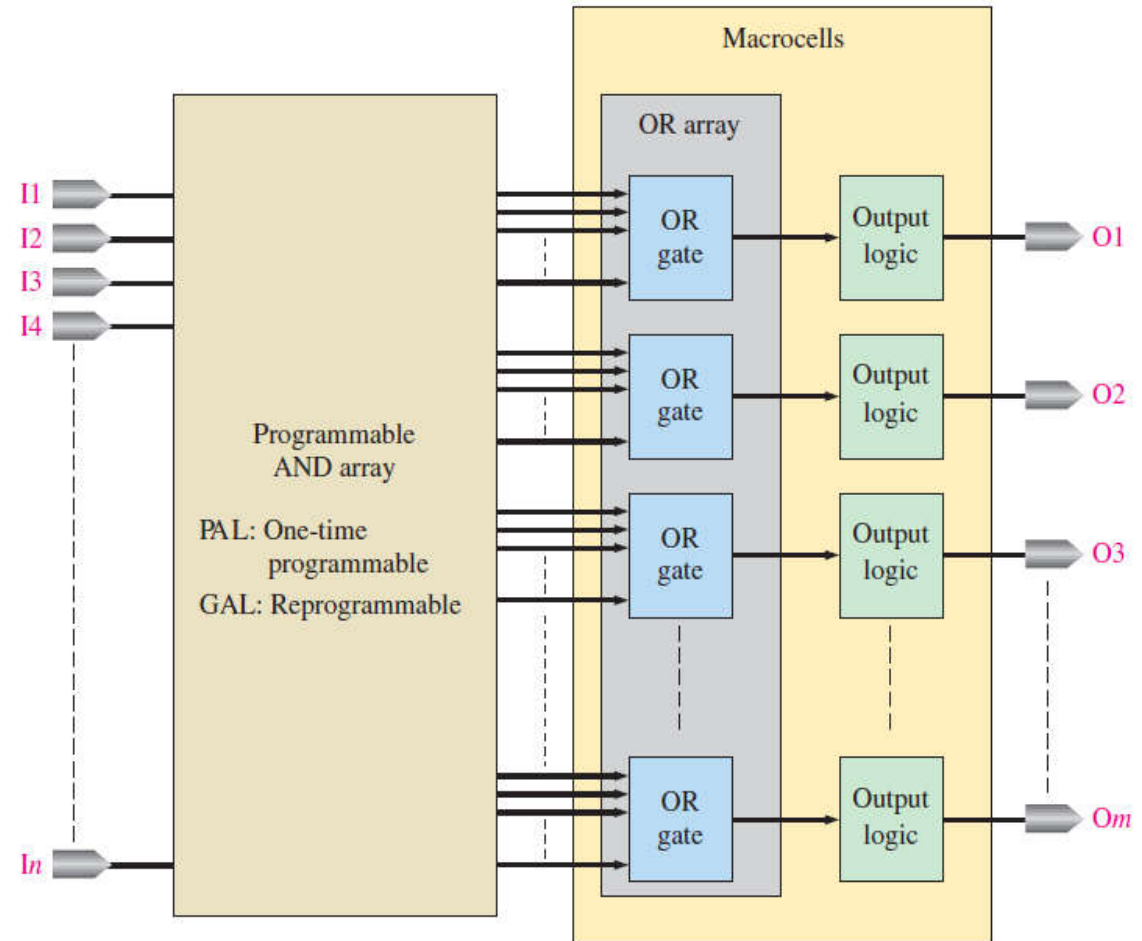
## Generic Block Diagram for PAL/GAL

- The AND array is programmable.
- For PAL the AND array is one time programmable.
- For GAL the AND array is reprogrammable.
- The programmable AND array outputs go to fixed OR gates.
- OR gates are connected to additional output logic.
- An OR gate combined with Output logic is called Macro-cell.
- In GAL Macro-cell is often reprogrammable.




## ■ CPLD

- Complex Programmable Logic Devices (CPLD)
- SPLDs (PLA, PAL) are limited in size due to the small number of input and output pins and the limited number of product terms
  - Combined number of inputs + outputs < 32 or so
- CPLDs contain multiple circuit blocks on a single chip
  - Each block is like a PAL: PAL-like block
  - Connections are provided between PAL-like blocks via an interconnection network that is programmable
  - Each block is connected to an I/O block as well




## ■ Structure of a CPLD

 
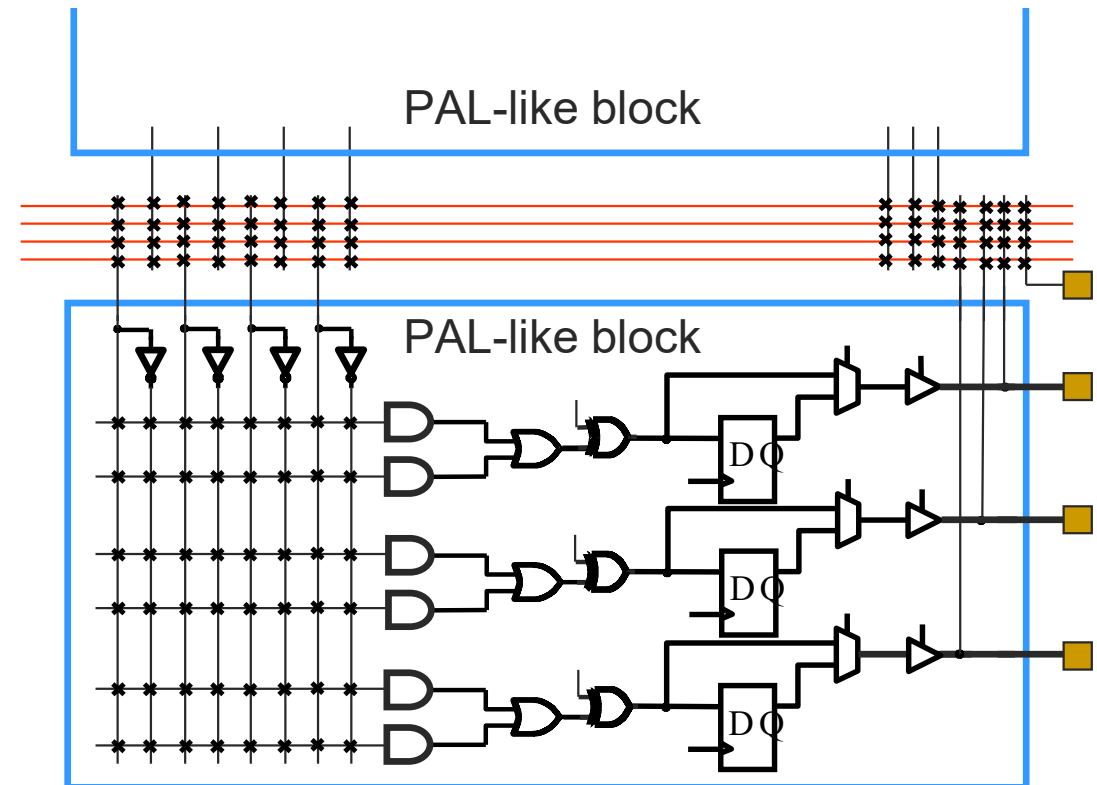
# Internal Structure of a PAL-like Block

- Includes macrocells
  - Usually about 16 each
- Fixed OR planes
  - OR gates have fan-in between 5-20
- XOR gates provide negation ability
  - XOR has a control input



## ■ More on PAL-like Blocks

- CPLD pins are provided to control XOR, MUX, and tri-state gates
- When tri-state gate is disabled, the corresponding output pin can be used as an input pin
  - The associated PAL-like block is then useless
- The AND plane and interconnection network are programmable
- Commercial CPLDs have between 2-100 PAL-like blocks



## Reference:

- [1] Thomas L. Floyd, “Digital Fundamentals” 11th edition, Prentice Hall.
- [2] M. Morris Mano, “Digital Logic & Computer Design” Prentice Hall.
- [3] Mixed contents from Vahid And Howard.






# Thanks


 
## ■ Programming a CPLD

- CPLDs have many pins – large ones have  $> 200$
- Removal of CPLD from a PCB is difficult without breaking the pins
  - Use ISP (in system programming) to program the CPLD
  - JTAG (Joint Test Action Group) port used to connect the CPLD to a computer




## ■ Example CPLD

- Use a CPLD to implement the function

■  $f = x_1x_3x_6' + x_1x_4x_5x_6' + x_2x_3x_7 + x_2x_4x_5x_7$

(from interconnection wires)

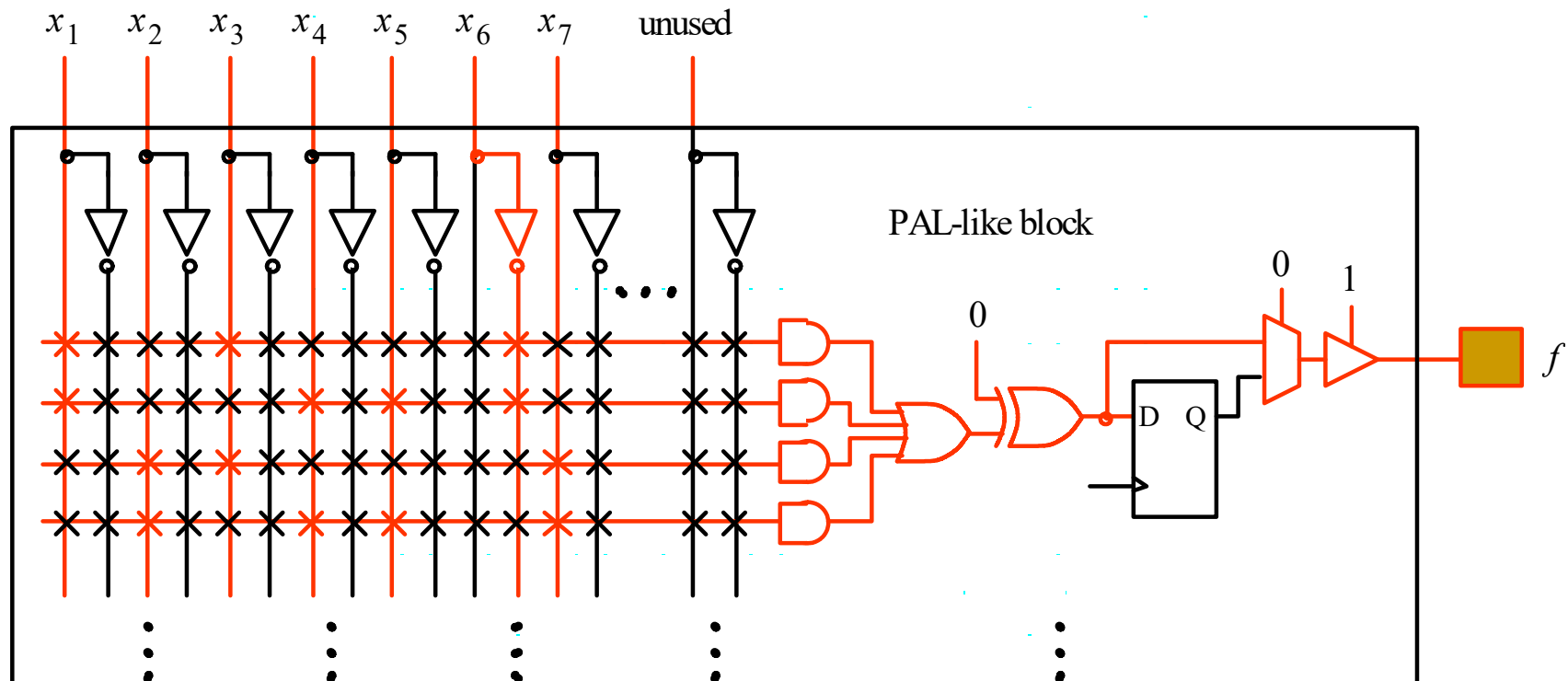


## ■ FPGA

- SPLDs and CPLDs are relatively small and useful for simple logic devices
  - Up to about 20000 gates
- Field Programmable Gate Arrays (FPGA) can handle larger circuits
  - No AND/OR planes
  - Provide logic blocks, I/O blocks, and interconnection wires and switches
  - Logic blocks provide functionality
  - Interconnection switches allow logic blocks to be connected to each other and to the I/O pins




# Structure of an FPGA

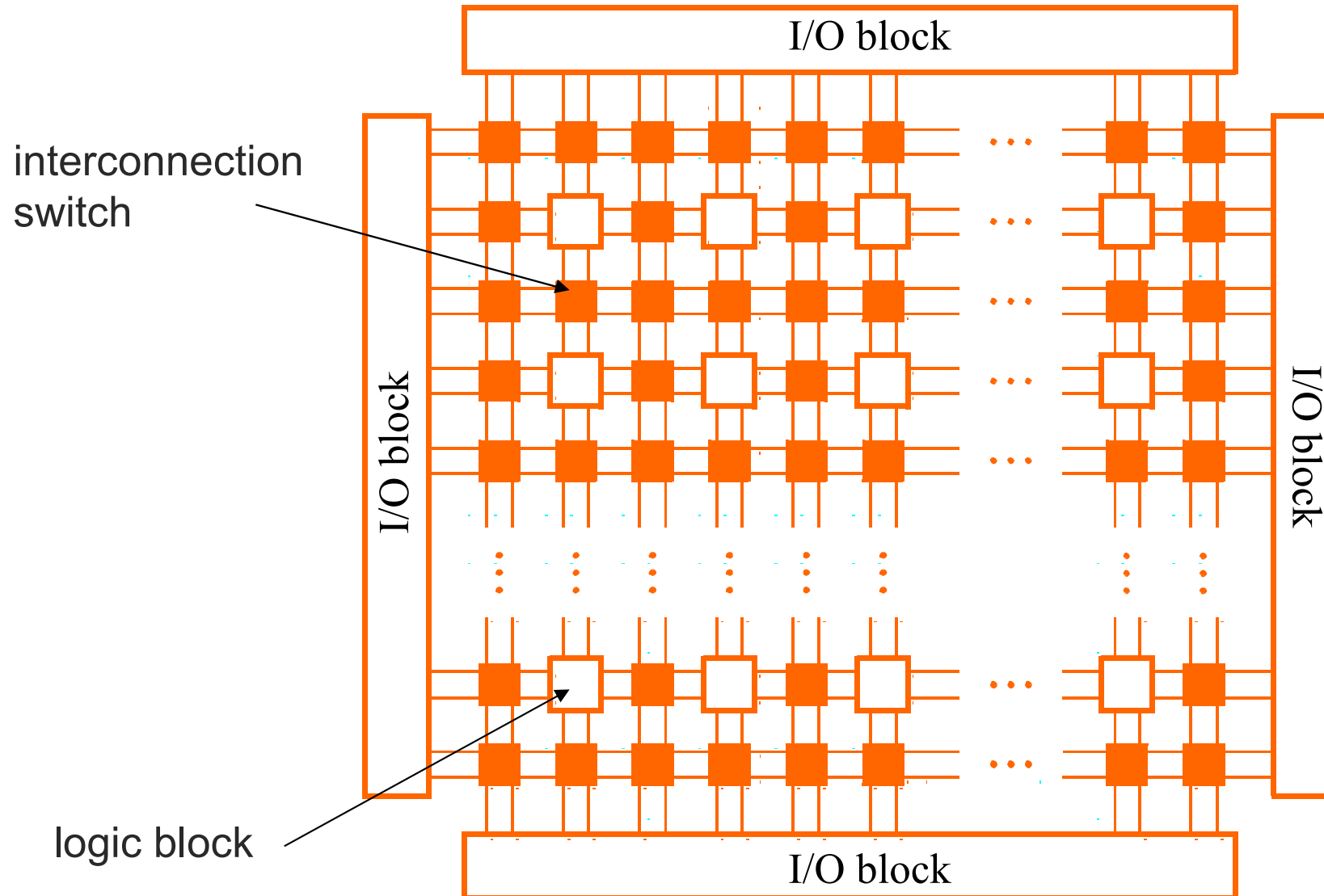
 
## ■ LUTs

- Logic blocks are implemented using a lookup table (LUT)
  - Small number of inputs, one output
  - Contains storage cells that can be loaded with the desired values
  - A 2 input LUT uses 3 MUXes to implement any desired function  $x_1$  of 2 variables
    - Shannon's expansion at work!




# Example 2 Input LUT

$x_1$	$x_2$	$f$
0	0	1
0	1	0
1	0	0
1	1	1

$f = x_1'x_2' + x_1x_2$ , or using Shannon's expansion:


$$f = x_1'(x_2') + x_1(x_2)$$
 
$$= x_1'(x_2'(1) + x_2(0)) + x_1(x_2'(0) + x_2(1))$$


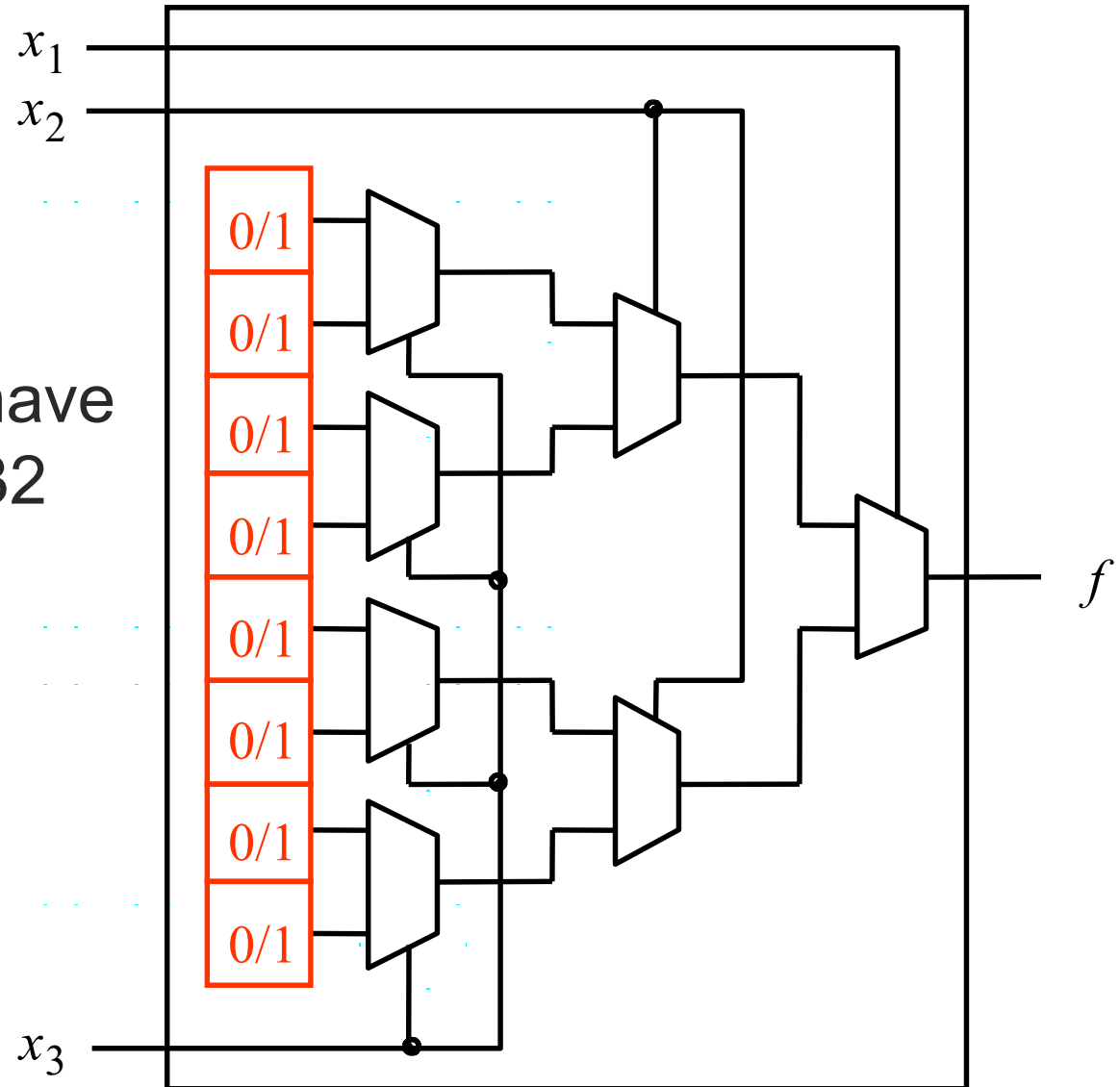
## ■ 3 Input LUT

- 7 2x1 MUXes and 8 storage cells are required
- Commercial LUTs have 4-5 inputs, and 16-32 storage cells




# ■ Programming an FPGA

- ISP method is used
- LUTs contain volatile storage cells
  - None of the other PLD technologies are volatile
  - FPGA storage cells are loaded via a PROM when power is first applied
- The UP2 Education Board by Altera contains a JTAG port, a MAX 7000 CPLD, and a FLEX 10K FPGA
  - The MAX 7000 CPLD chip is EPM7128SLC84-7
  - EPM7 → MAX 7000 family; 128 macrocells; LC84 → 84 pin PLCC package; 7 → speed grade
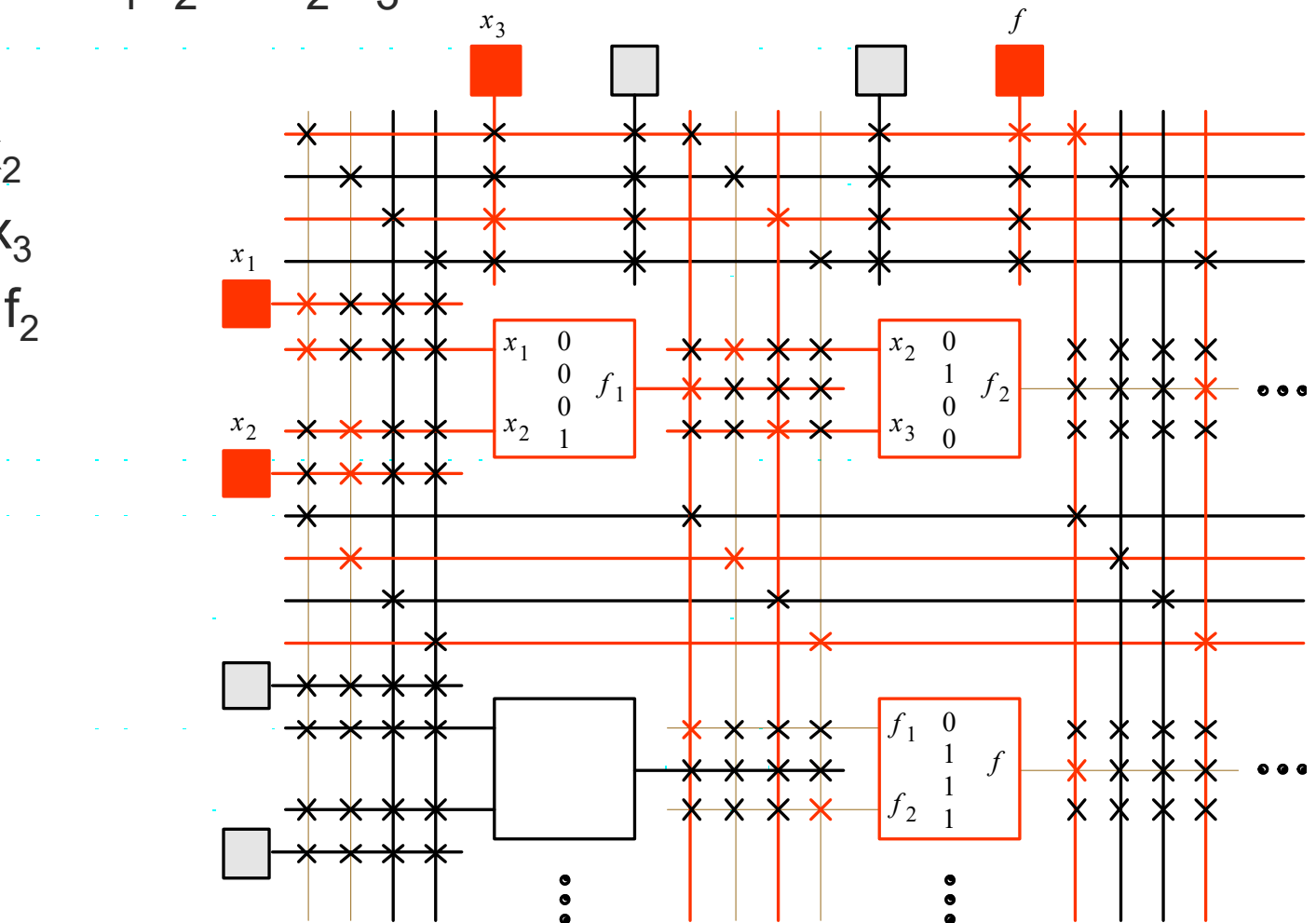
# Example FPGA

- Use an FPGA with 2 input LUTS to implement the function  $f = x_1x_2 + x_2'x_3$

- $f_1 = x_1x_2$
- $f_2 = x_2'x_3$
- $f = f_1 + f_2$




## ■ Another Example FPGA

- Use an FPGA with 2 input LUTS to implement the function  $f = x_1x_3x_6' + x_1x_4x_5x_6' + x_2x_3x_7 + x_2x_4x_5x_7$

- Fan-in of expression is too large for FPGA (this was simple to do in a CPLD)
- Factor f to get sub-expressions with max fan-in = 2
  - $f = x_1x_6'(x_3 + x_4x_5) + x_2x_7(x_3 + x_4x_5)$   
 $= (x_1x_6' + x_2x_7)(x_3 + x_4x_5)$
- Could use Shannon's expansion instead
  - Goal is to build expressions out of 2-input LUTs

# FPGA Implementation

$$f = (x_1x_6' + x_2x_7)(x_3 + x_4x_5)$$

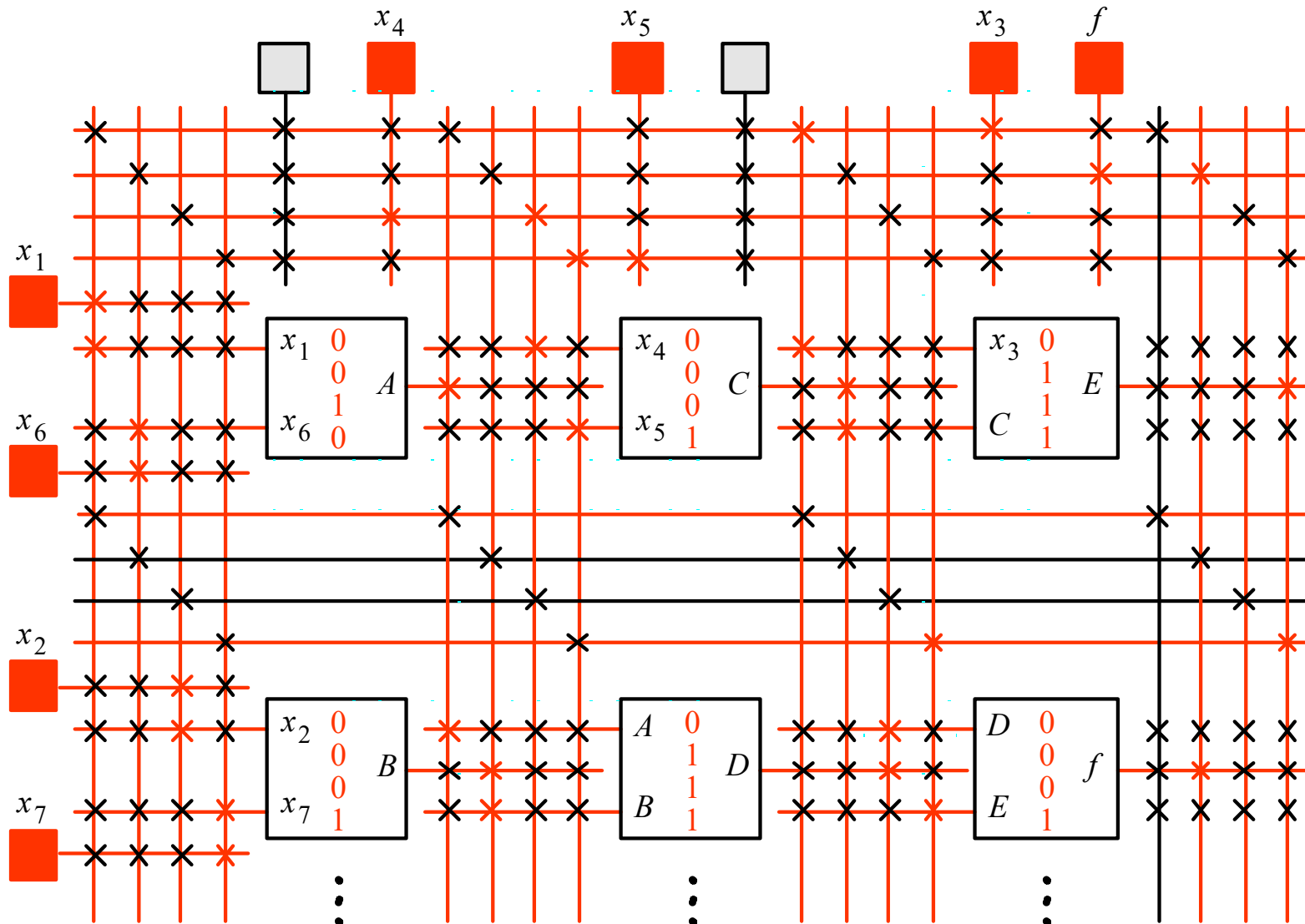




# ■ Custom Chips

- PLDs are limited by number of programmable switches
  - Consume space
  - Reduce speed
- Custom chips are created from scratch
  - Expensive → used when high speed is required, volume sales are expected, and chip size is small but with high density of gates
  - ASICs (Application Specific Integrated Circuits) are custom chips that use a standard cell layout to reduce design costs

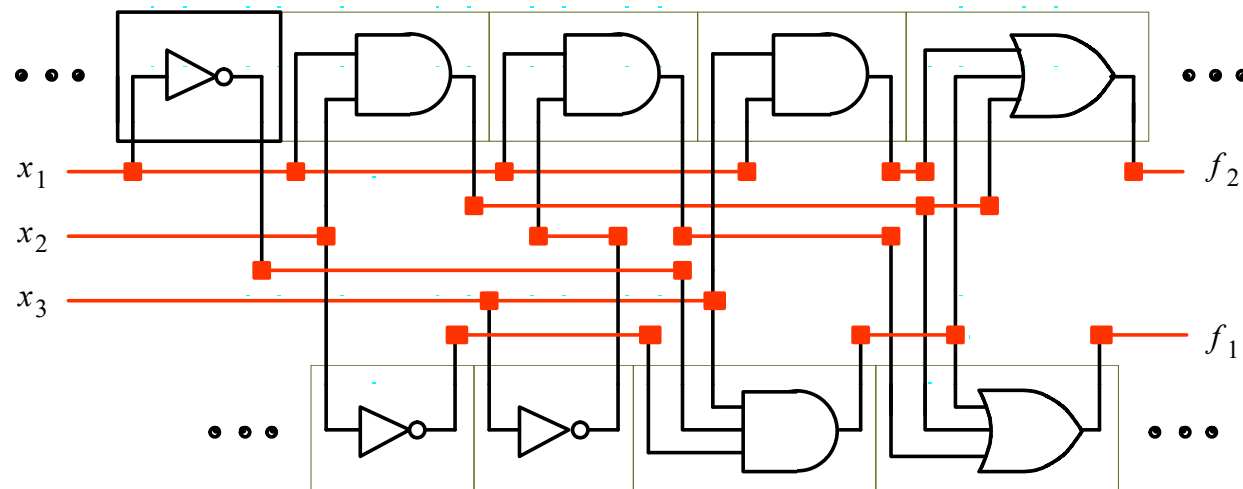
# Standard Cells

- Rows of logic gates can be connected by wires in the *routing channels*
  - Designers (via CAD tools) select prefab gates from a library and place them in rows
  - Interconnections are made by wires in routing channels
    - Multiple layers may be used to avoid short circuiting
    - A hard-wired connection between layers is called a *via*



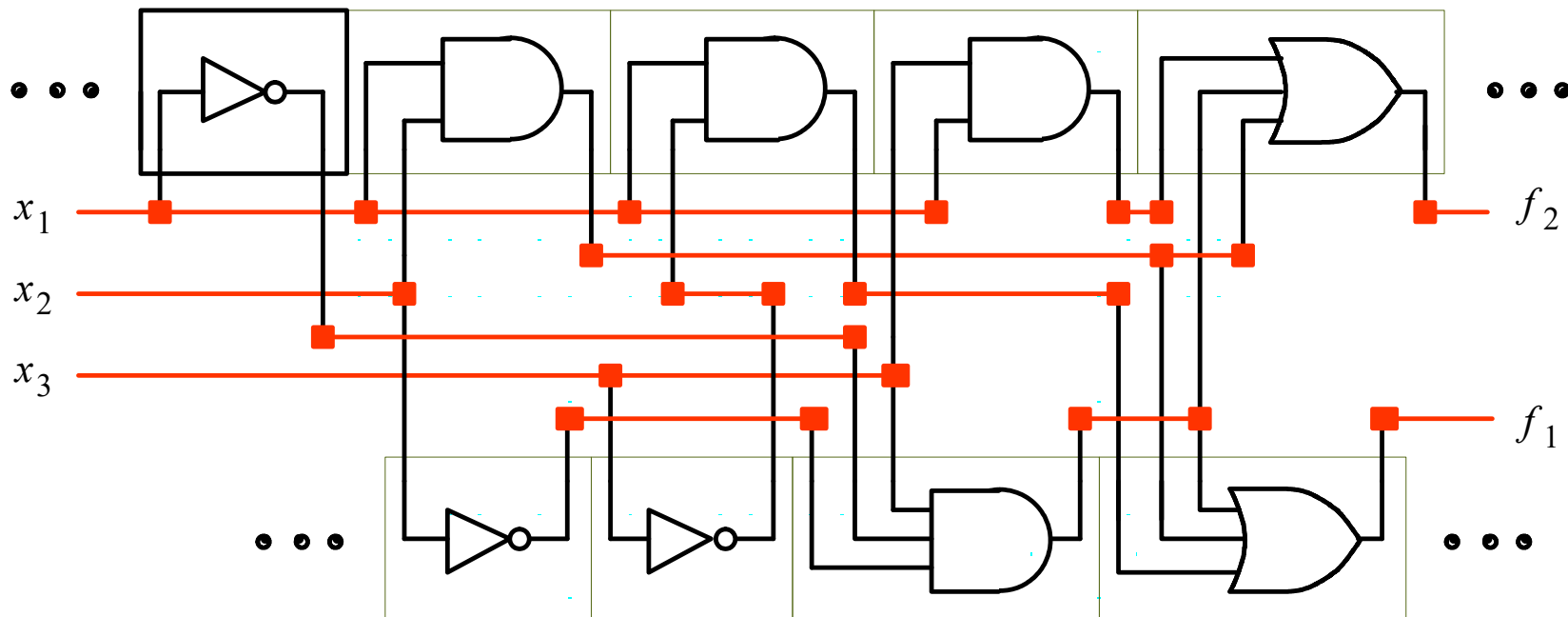
## ■ Example: Standard Cells

- $f_1 = x_1x_2 + x_1'x_2'x_3 + x_1x_3'$
- $f_2 = x_1x_2 + x_1'x_2'x_3 + x_1x_3$



 
## ■ Sea of Gates Gate Array

- A Sea of Gates gate array is just like a standard cell except all gates are of the same type
  - Interconnections are run in channels and use multiple layers
  - Cheaper to manufacture due to regularity



# Example: Sea of Gates

$f_1 = x_2x_3' + x_1x_3$

 

# ■ Digital Logic Technology Tradeoffs

