



EEE 3101: Digital Logic and Circuits

Counters

Course Teacher: Nafiz Ahmed Chisty

Head, Department of EEE

Associate Professor, Department of EEE & CoE


Faculty of Engineering

Room# D0105, D Building

Email: chisty@aiub.edu

Website: <http://engg.aiub.edu/faculties/nafiz>


Website: www.nachisty.com

 

Counters


Asynchronous Counter

 Flip-flops (FF) **do not** have a **common clock pulse**



Synchronous Counter

 Flip-flops (FF) **have** a **common clock pulse**





Asynchronous Counter

An asynchronous counter is one in which the flip-flops (FF) within the counter do not change states at exactly the same time because they **do not have a common clock pulse**

Asynchronous Counter Operation



- Asynchronous binary counter
 - 2-bit asynchronous binary counter
 - 3-bit asynchronous binary counter
 - 4-bit asynchronous binary counter
- Asynchronous decade counter
- Asynchronous Modulus Twelve counter

2-bit asynchronous binary counter

 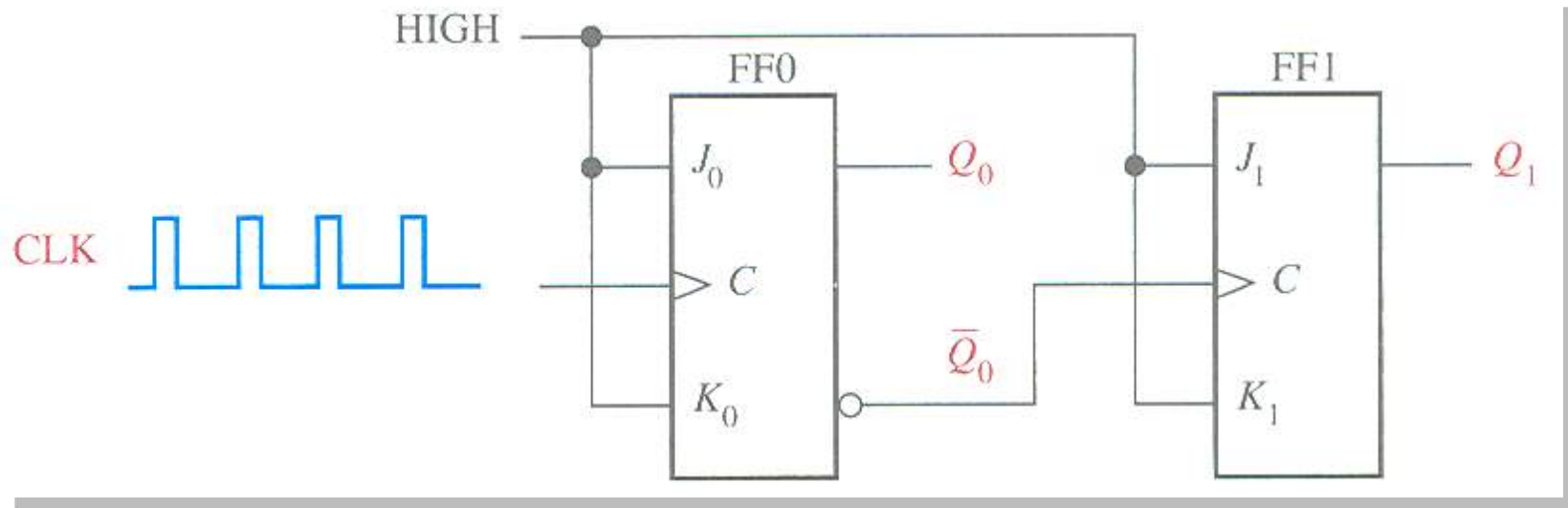


CLOCK PULSE	Q_1	Q_0
Initially	0	0
1	0	1
2	1	0
3	1	1
4 (recycles)	0	0

2-bit asynchronous binary counter

  


CLOCK PULSE	Q_1	Q_0
Initially	0	0
1	0	1
2	1	0
3	1	1
4 (recycles)	0	0

3-bit asynchronous binary counter

 

CLOCK PULSE	Q_2	Q_1	Q_0
Initially	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
8 (recycles)	0	0	0

 

Modulus of a Counter

The **modulus** of a counter is the number of unique states through which the counter will sequence. The maximum possible number of states (maximum modulus) of a counter is 2^n , where n is the number of flip-flops in the counter. Counters can be designed to have a number of states in their sequence that is less than the maximum of 2^n . This type of sequence is called a *truncated sequence*.

Asynchronous decade (MOD-10) counter


One common modulus for counters with truncated sequences is ten (called MOD10). Counters with ten states in their sequence are called **decade** counters. A decade counter with a count sequence of zero (0000) through nine (1001) is a BCD decade counter because its ten-state sequence produces the BCD code. This type of counter is useful in display applications in which BCD is required for conversion to a decimal readout.

DECIMAL	BINARY
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
8	1000
9	1001
10	1010
11	1011
12	1100
13	1101
14	1110
15	1111


Not wanted. We want 0000.
So Decode this state.

To obtain a truncated sequence, it is necessary to force the counter to recycle before going through all of its possible states. For example, the BCD decade counter must recycle back to the 0000 state after the 1001 state. A decade counter requires four flip-flops (three flip-flops are insufficient because $2^3 = 8$).

Asynchronous decade counter

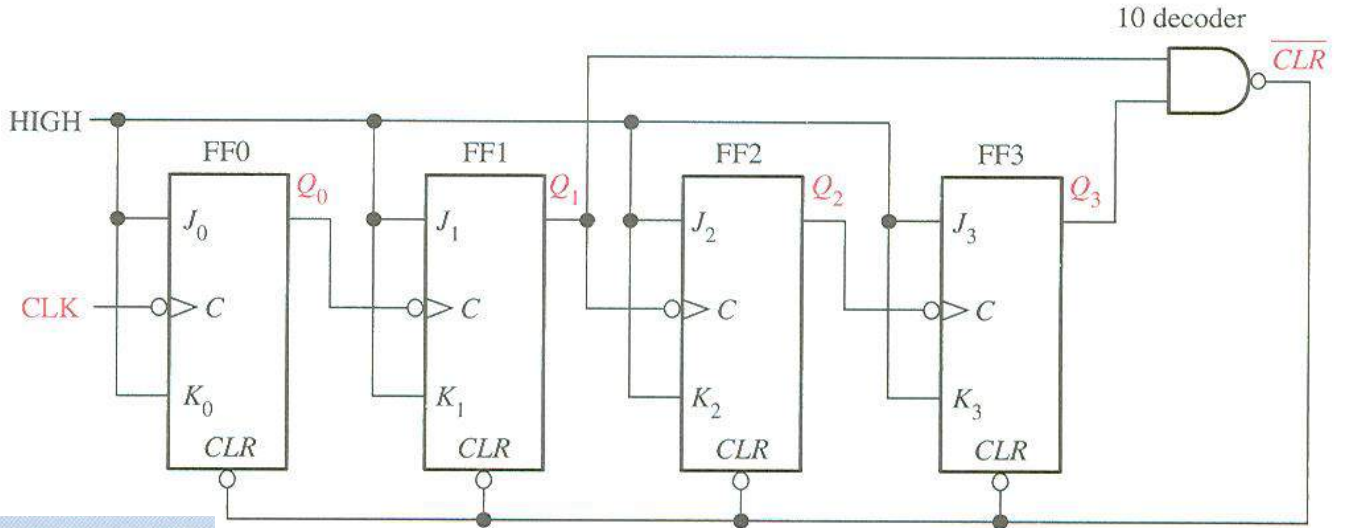

DECIMAL	BINARY
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
8	1000
9	1001
10	1010
11	1011
12	1100
13	1101
14	1110
15	1111

 

Asynchronous Modulus Twelve counter

Q_3 Q_2 Q_1 Q_0

0 0 0 0

. . . .

. . . .

. . . .


1 0 1 1



1 1 0 0

Recycles

Normal next state So Decode this state.

Already ZERO, so no need to ACTIVE Clear

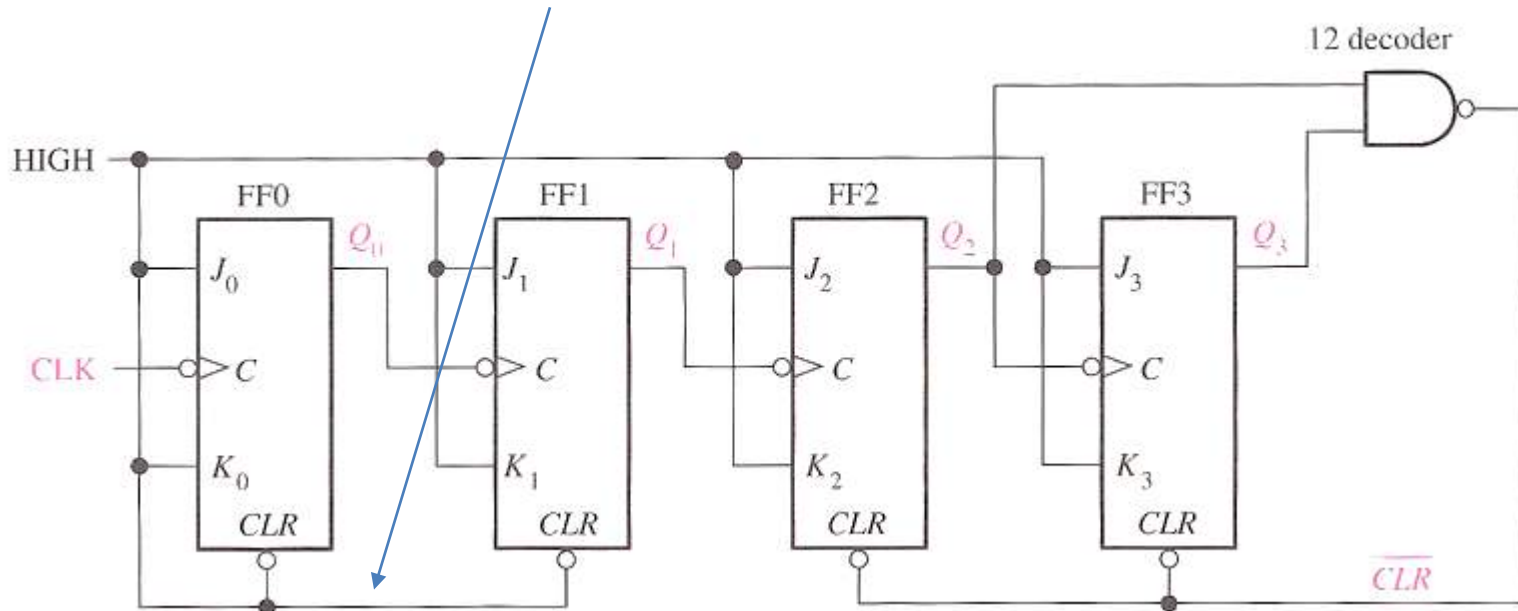

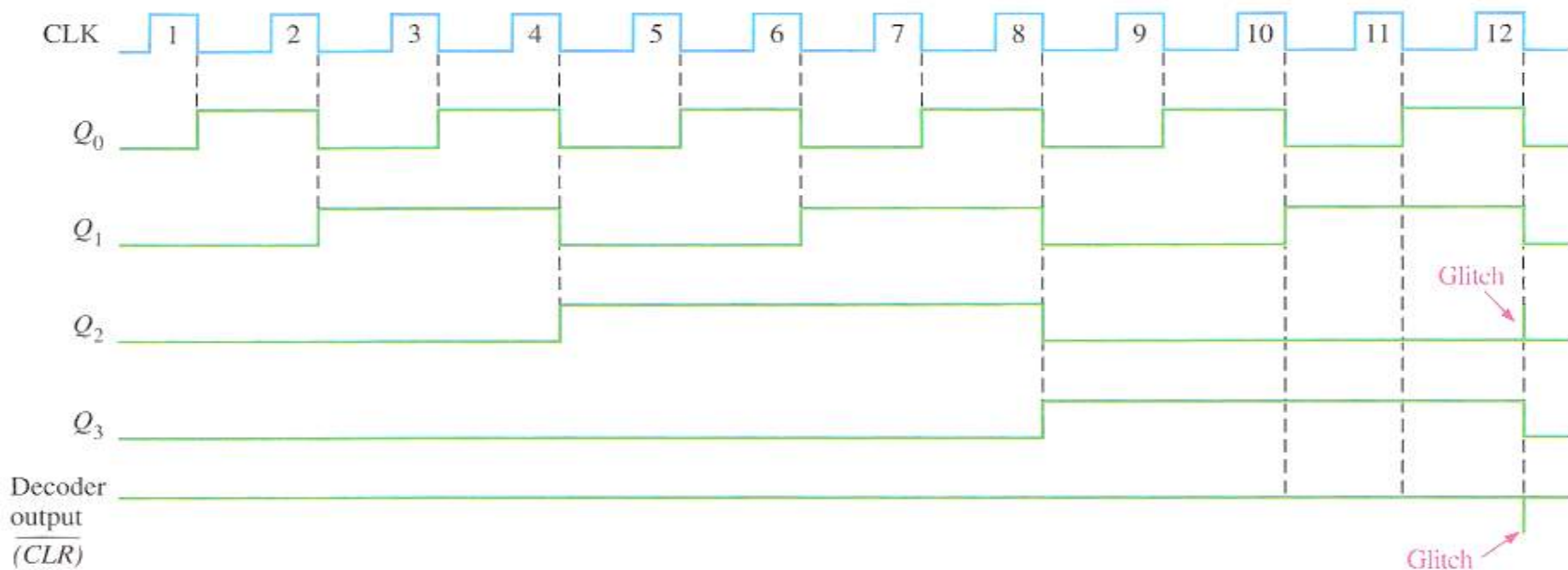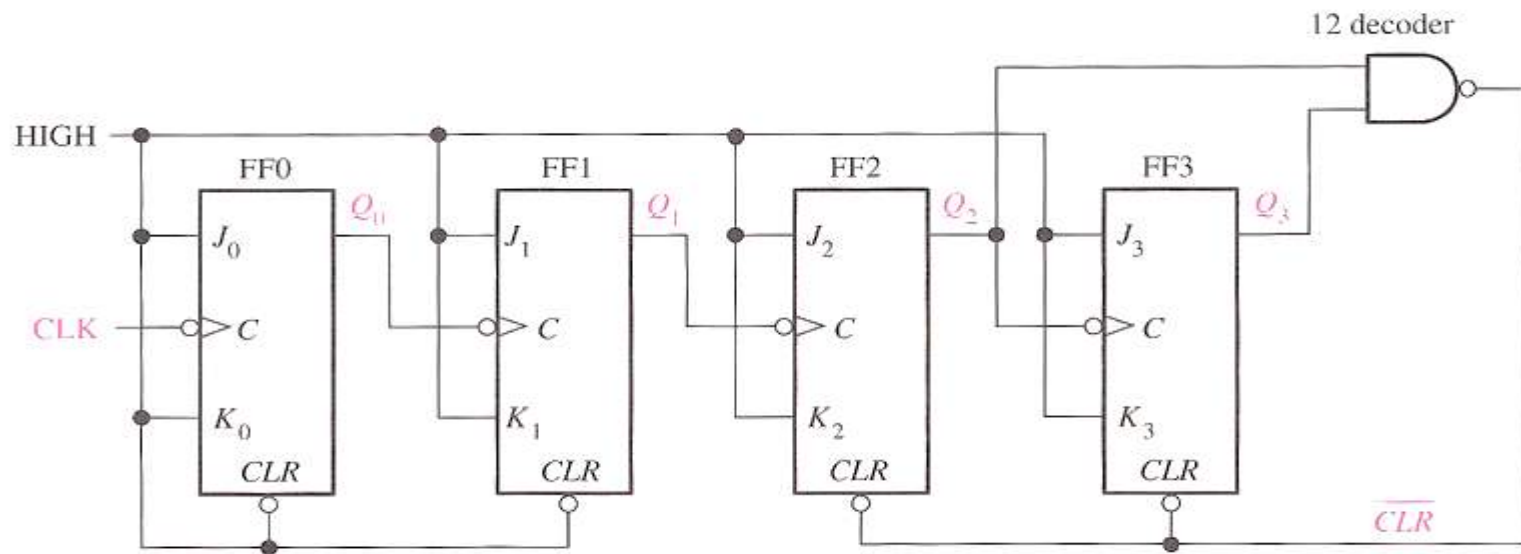

Glitch


Synchronous Counter


A Synchronous counter is one in which the flip-flops (FF) within the counter are clocked at the same time by a common clock pulse.

Synchronous Counter Operation

- Synchronous binary counters
 - 2-bit counter
 - 3-bit counter
 - 4-bit counter
- Synchronous BCD Decade counter
- Irregular sequence counter



2-bit synchronous binary counter

 

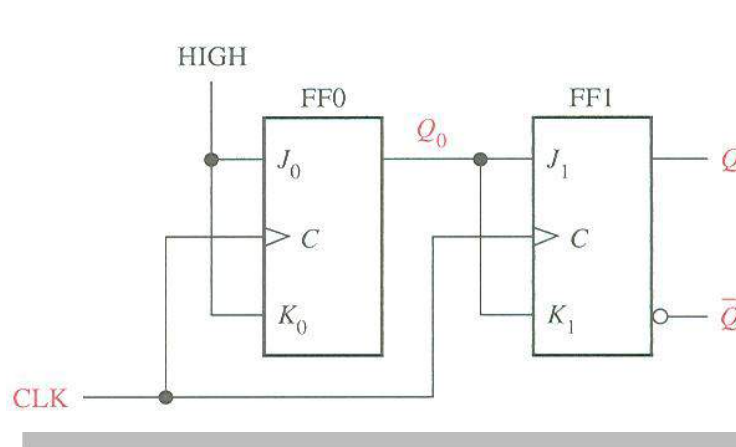


$$J_0 = K_0 = 1$$



$$J_1 = K_1 = Q_0$$

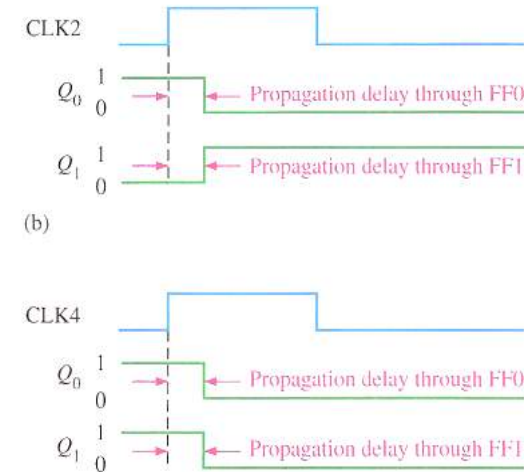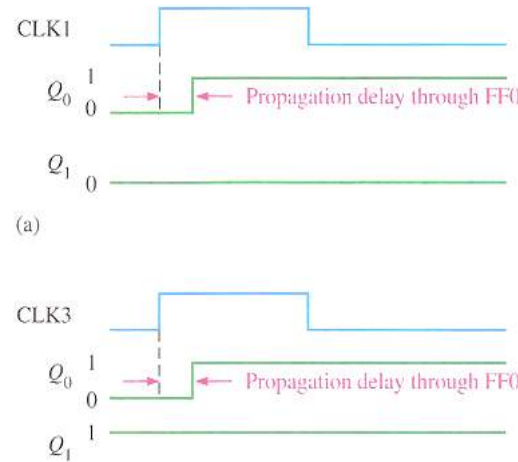

Q_1	Q_0
0	0
0	1
1	0
1	1
0	0

 


3-bit synchronous binary counter

  

CLOCK PULSE	Q_2	Q_1	Q_0
Initially	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
8 (recycles)	0	0	0

4-bit synchronous binary counter

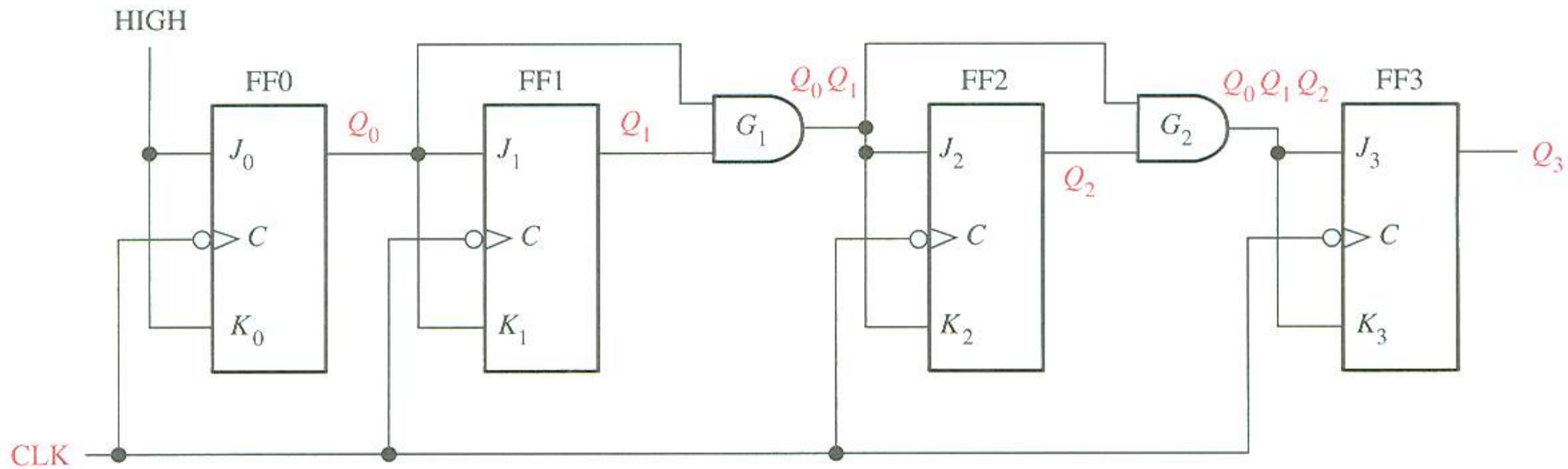


DECIMAL	BINARY
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
8	1000
9	1001
10	1010
11	1011
12	1100
13	1101
14	1110
15	1111

$$J_0 = K_0 = 1$$

$$J_1 = K_1 = Q_0$$

$$J_2 = K_2 = Q_0Q_1$$

$$J_3 = K_3 = Q_0Q_1Q_2$$

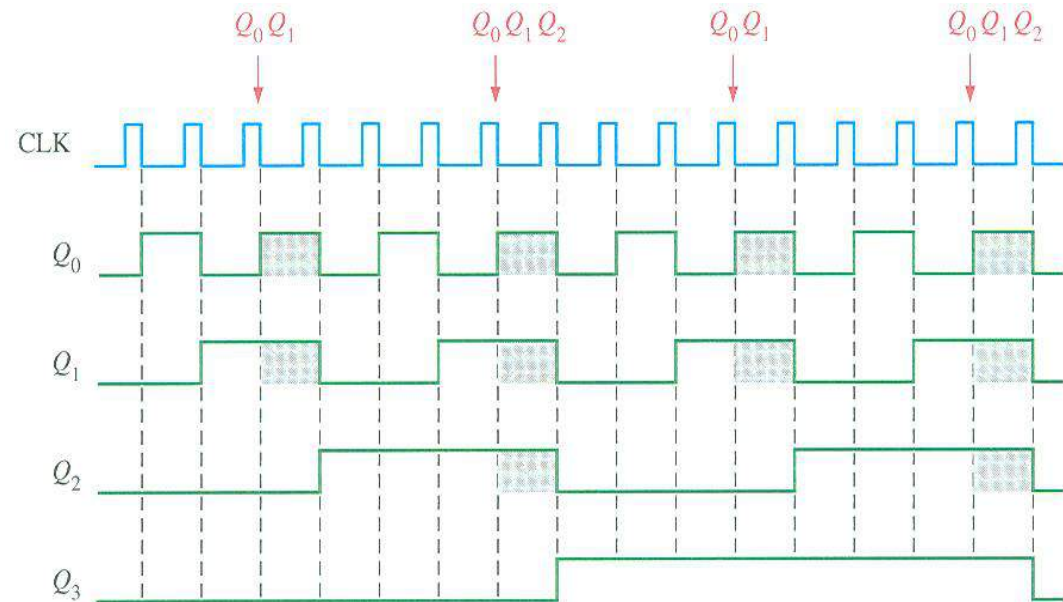

Synchronous Decade counter (MOD 10)

4-bit synchronous binary counter


$$J_0 = K_0 = 1$$

$$J_1 = K_1 = Q_0$$


$$J_2 = K_2 = Q_0 Q_1$$

$$J_3 = K_3 = Q_0 Q_1 Q_2$$

Forcefully Stable

 

Forcefully Toggle

 

Naturally Zero (unchanged)

9

$Q_3 Q_2 Q_1 Q_0$

1001

10

1010

0

0000

Forcefully Toggle

Forcefully Stable


$$J_0 = K_0 = 1$$

$$J_1 = K_1 = Q_0 \bar{Q}_3$$

$$J_2 = K_2 = Q_0 Q_1$$

$$J_3 = K_3 = Q_0 Q_1 Q_2 + Q_0 Q_3$$

Synchronous BCD decade counter

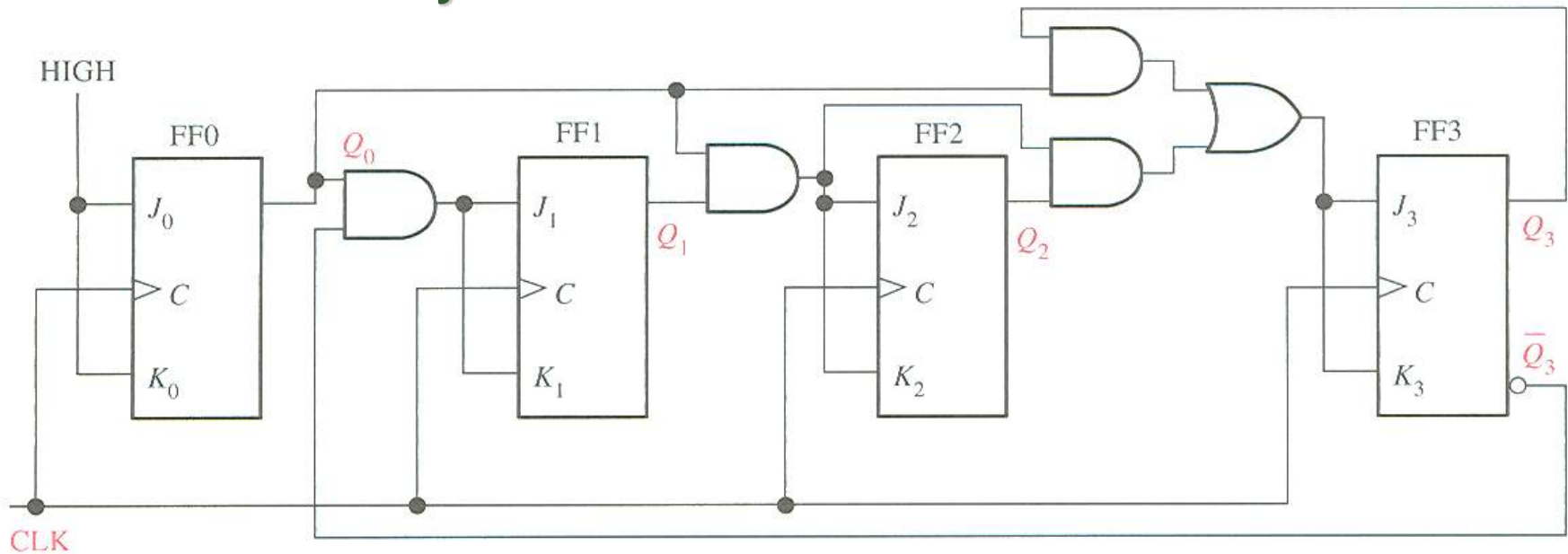


$$J_0 = K_0 = 1$$

$$J_1 = K_1 = Q_0 \overline{Q_3}$$

$$J_2 = K_2 = Q_0 Q_1$$


$$J_3 = K_3 = Q_0 Q_1 Q_2 + Q_0 Q_3$$

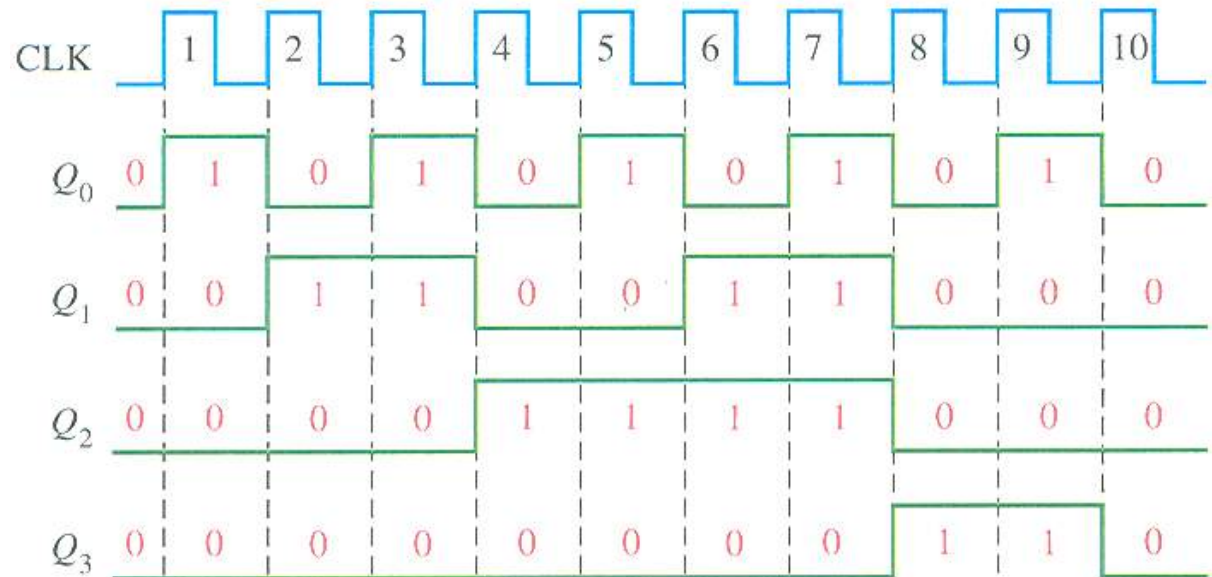

DESIGN OF SYNCHRONOUS COUNTERS

In this section, you will see how sequential circuit design techniques can be applied specifically to counter design. In general, sequential circuits can be classified into two types: (1) those in which the output or outputs depend only on the present internal state (called *Moore circuits*) and (2) those in which the output or outputs depend on both the present state and the input or inputs (called *Mealy circuits*). This section is

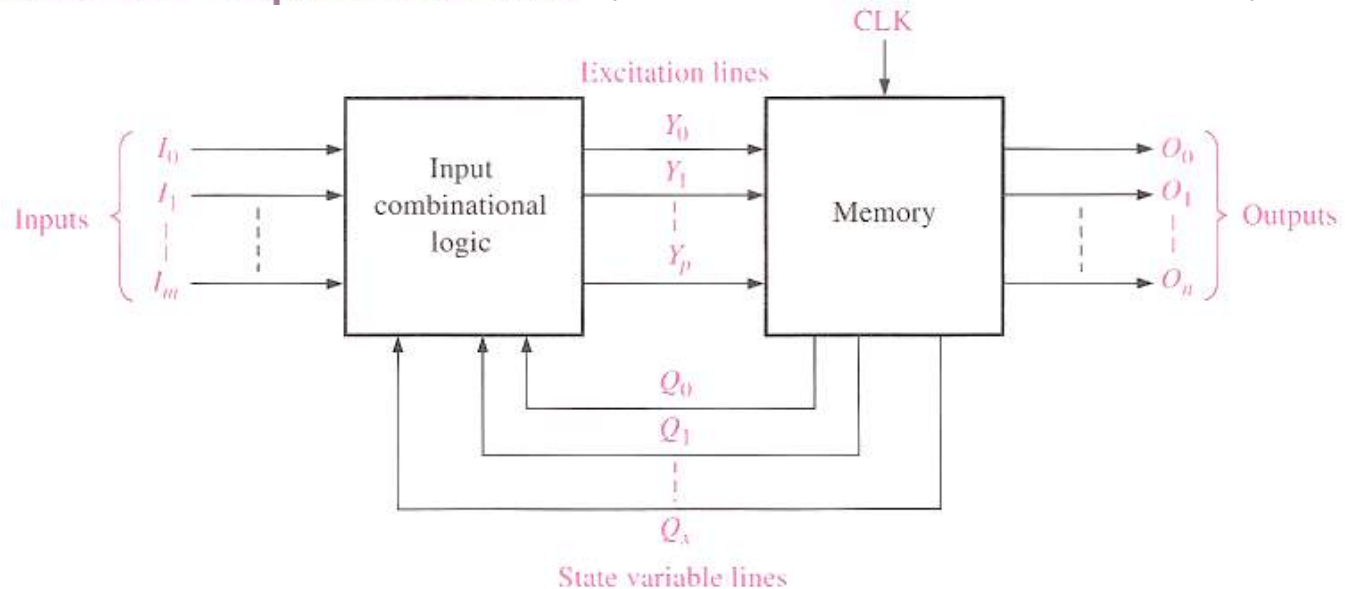
General Model of a Sequential Circuit (sequential circuit or state machine)



Not all sequential circuits have input and output variables as in the general model just discussed. However, all have excitation variables and state variables. Counters are a special case of clocked sequential circuits. In this section, a general design procedure for sequential circuits is applied to synchronous counters in a series of steps.


Step 1: State Diagram

 The first step in the design of a counter is to create a state diagram. A **state diagram** shows the progression of states through which the counter advances when it is clocked. As an example, Figure 8–28 is a state diagram for a basic 3-bit Gray code counter. This particular circuit has no inputs other than the clock and no outputs other than the outputs taken off each flip-flop in



Step 2: Next-State Table

Once the sequential circuit is defined by a state diagram, the second step is to derive a next-state table, which lists each state of the counter (present state) along with the corresponding next state. *The next state is the state that the counter goes to from its present state upon application of a clock pulse.* The next-state table is derived from the state diagram and is shown in Table 8–7 for the 3-bit Gray code counter. Q_0 is the least significant bit.

 


PRESENT STATE			NEXT STATE		
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0
0	0	0	0	0	1
0	0	1	0	1	1
0	1	1	0	1	0
0	1	0	1	1	0
1	1	0	1	1	1
1	1	1	1	0	1
1	0	1	1	0	0
1	0	0	0	0	0

Step 3: Flip-Flop Transition Table

Table 8–8 is a transition table for the J-K flip-flop. All possible output transitions are listed by showing the Q output of the flip-flop going from present states to next states. Q_N is the present state of the flip-flop (before a clock pulse) and Q_{N+1} is the next state (after a clock pulse). For each output transition, the J and K inputs that will cause the transition to occur are listed. An X indicates a “don’t care” (the input can be either a 1 or a 0).

OUTPUT TRANSITIONS			FLIP-FLOP INPUTS	
Q_N		Q_{N+1}	J	K
0	→	0	0	X
0	→	1	1	X
1	→	0	X	1
1	→	1	X	0

 Q_N : present state Q_{N+1} : next state X: “don’t care”




To design the counter, the transition table is applied to each of the flip-flops in the counter, based on the next-state table (Table 8–7). For example, for the present state 000, Q_0 goes from a present state of 0 to a next state of 1. To make this happen, J_0 must be a 1 and you don’t care what K_0 is ($J_0 = 1$, $K_0 = X$), as you can see in the transition table (Table 8–8). Next, Q_1 is 0 in the present state and remains a 0 in the next state. For this transition, $J_1 = 0$ and $K_1 = X$. Finally, Q_2 is 0 in the present state and remains a 0 in the next state. Therefore, $J_2 = 0$ and $K_2 = X$. This analysis is repeated for each present state in Table 8–7.

Step 4: Karnaugh Maps

Karnaugh maps can be used to determine the logic required for the J and K inputs of each flip-flop in the counter. There is a Karnaugh map for the J input and a Karnaugh map for the K input of each flip-flop. In this design procedure, each cell in a Karnaugh map represents one of the present states in the counter sequence listed in Table 8–7.

From the J and K states in the transition table (Table 8–8) a 1, 0, or X is entered into each present state cell on the maps depending on the transition of the Q output for a particular flip-flop. To illustrate this procedure, two sample entries are shown for the J_0 and the K_0 inputs to the least significant flip-flop (Q_0) in Figure 8–29.

For Q_0 :

 

The values of J_0 and K_0 required to produce the transition are placed on each map in the present-state cell.

The values of J_0 and K_0 required to produce the transition are placed on each map in the present-state cell.

J_0 map

Q_2Q_1	Q_0	0	1
00		1	
01			
11			
10			X

K_0 map

Q_2Q_1	Q_0	0	1
00		1	
01			
11			
10			1

Q_2Q_1	Q_0	0	1
00		1	X
01		0	X
11		1	X
10		0	X

J_0 map

Q_2Q_1	Q_0	0	1
00		X	0
01		X	1
11		X	0
10		X	1

K_0 map

Output Transitions	Flip-Flop Inputs
Q_N Q_{N+1}	J K
0 → 0	0 X
0 → 1	1 X
1 → 0	X 1
1 → 1	X 0

Flip-flop transition table

Present State	Next State
Q_2 Q_1 Q_0	Q_2 Q_1 Q_0
0 0 0	0 0 1
0 0 1	0 1 1
0 1 1	0 1 0
0 1 0	1 1 0
1 1 0	1 1 1
1 1 1	1 0 1
1 0 1	1 0 0
1 0 0	0 0 0



Next-state table

For the present state 000, Q_0 makes a transition from 0 to 1 to the next state.



For the present state 101, Q_0 makes a transition from 1 to 0 to the next state.

The completed Karnaugh maps for all three flip-flops in the counter are shown in Figure 8–30. The cells are grouped as indicated and the corresponding Boolean expressions for each group are derived.



For Q_2 :

  

For Q_1 :

  

For Q_0 :

  

Step 5: Logic Expressions for Flip-Flop Inputs

From the Karnaugh maps of Figure 8–30 you obtain the following expressions for the J and K inputs of each flip-flop:

$$\begin{aligned} J_0 &= Q_2 Q_1 + \overline{Q_2} \overline{Q_1} = \overline{Q_2} \oplus Q_1 \\ K_0 &= Q_2 \overline{Q_1} + \overline{Q_2} Q_1 = Q_2 \oplus Q_1 \end{aligned}$$

$$\begin{aligned} J_1 &= \overline{Q_2} Q_0 \\ K_1 &= Q_2 Q_0 \end{aligned}$$


$$\begin{aligned} J_2 &= Q_1 \overline{Q_0} \\ K_2 &= \overline{Q_1} \overline{Q_0} \end{aligned}$$



Implement in front of the flip-flops

Step 6: Counter Implementation

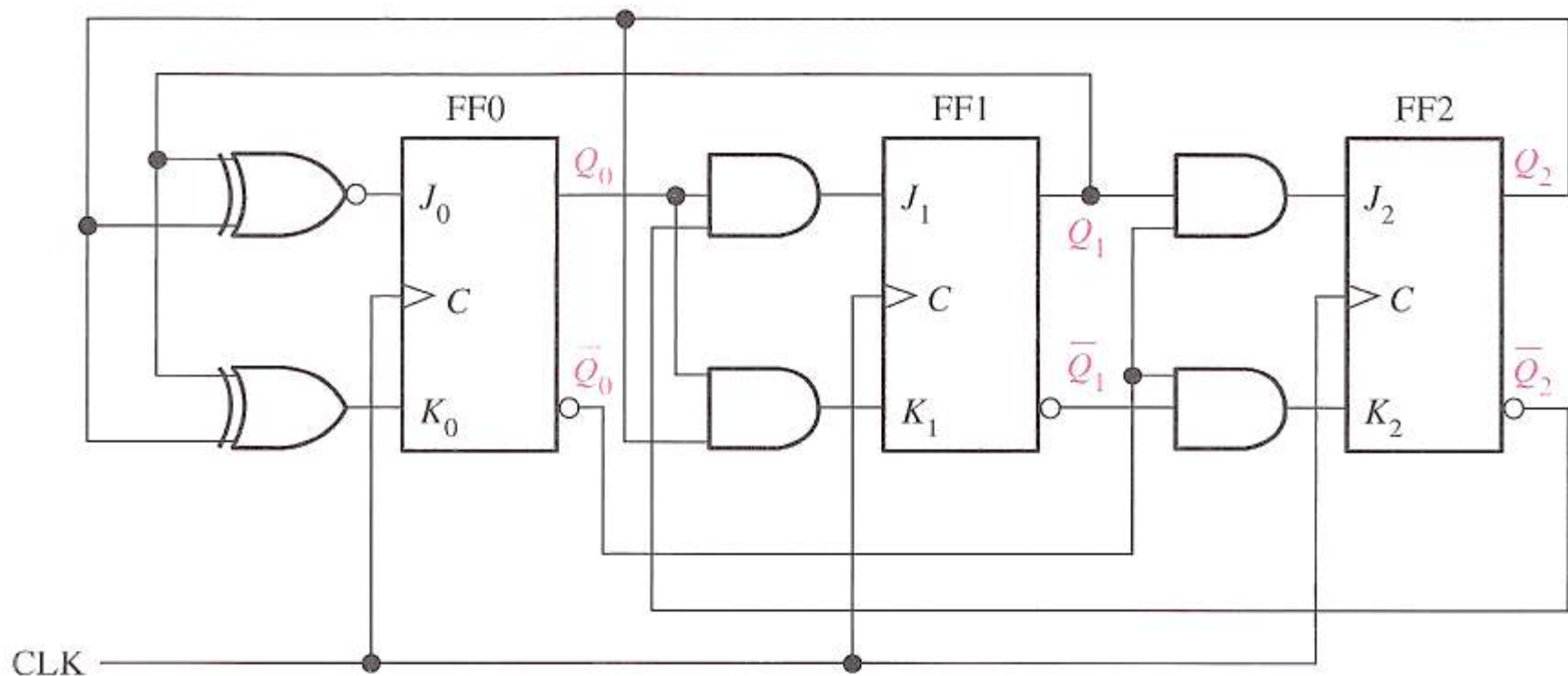The final step is to implement the combinational logic from the expressions for the J and K inputs and connect the flip-flops to form the complete 3-bit Gray code counter as shown in Figure 8–31.




Three-bit Gray code counter.

A summary of steps used in the design of this counter follows. In general, these steps can be applied to any sequential circuit.

1. Specify the counter sequence and draw a state diagram.
2. Derive a next-state table from the state diagram.
3. Develop a transition table showing the flip-flop inputs required for each transition. The transition table is always the same for a given type of flip-flop.
4. Transfer the J and K states from the transition table to Karnaugh maps. There is a Karnaugh map for each input of each flip-flop.
5. Group the Karnaugh map cells to generate and derive the logic expression for each flip-flop input.
6. Implement the expressions with combinational logic, and combine with the flip-flops to create the counter.

 EXAMPLE

Design a counter with the irregular binary count sequence shown in the state diagram of Figure 8–32. Use J-K flip-flops.



Solution

Step 1: The state diagram is as shown. Although there are only four states, a 3-bit counter is required to implement this sequence because the maximum binary count is seven. Since the required sequence does not include all the possible binary states, the invalid states (0, 3, 4, and 6) can be treated as “don’t cares” in the design. However, if the counter should erroneously get into an invalid state, you must make sure that it goes back to a valid state.


Step 2: The next-state table is developed from the state diagram and is given in Table 8–9.

PRESENT STATE			NEXT STATE		
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0
0	0	1	0	1	0
0	1	0	1	0	1
1	0	1	1	1	1
1	1	1	0	0	1


Step 3: The transition table for the J-K flip-flop is repeated in Table 8–10.

OUTPUT TRANSITIONS			FLIP-FLOP INPUTS	
Q_N		Q_{N+1}	J	K
0	→	0	0	X
0	→	1	1	X
1	→	0	X	1
1	→	1	X	0

 
Step 4: The J and K inputs are plotted on the present-state Karnaugh maps in Figure 8–33. Also “don’t cares” can be placed in the cells corresponding to the invalid states of 000, 011, 100, and 110, as indicated by the red Xs.




J_2 map

 


J_1 map

 


J_0 map

 

K_2 map

 

K_1 map

 

K_0 map

PRESENT STATE			NEXT STATE		
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0
0	0	1	0	1	0
0	1	0	1	0	1
1	0	1	1	1	1
1	1	1	0	0	1


The J and K inputs are plotted on the present-state Karnaugh maps in Figure 8–33. Also “don’t cares” can be placed in the cells corresponding to the invalid states of 000, 011, 100, and 110, as indicated by the red Xs.

EXAMPLE


Develop a synchronous 3-bit up/down counter with a Gray code sequence. The counter should count up when an $\overline{\text{UP/DOWN}}$ control input is 1 and count down when the control input is 0.

Solution

 Step 1: The state diagram is shown in Figure 8–35. The 1 or 0 beside each arrow indicates the state of the $\overline{\text{UP/DOWN}}$ control input, Y .



Next-State Table

 

PRESENT STATE			NEXT STATE					
			Y = 0 (DOWN)			Y = 1 (UP)		
Q ₂	Q ₁	Q ₀	Q ₂	Q ₁	Q ₀	Q ₂	Q ₁	Q ₀
0	0	0	1	0	0	0	0	1
0	0	1	0	0	0	0	1	1
0	1	1	0	0	1	0	1	0
0	1	0	0	1	1	1	1	0
1	1	0	0	1	0	1	1	1
1	1	1	1	1	0	1	0	1
1	0	1	1	1	1	1	0	0
1	0	0	1	0	1	0	0	0

$Y = \overline{\text{UP/DOWN}}$ control input.







Step 3: The transition table for the J-K flip-flops is repeated in Table 8–12.

OUTPUT TRANSITIONS			FLIP-FLOP INPUTS	
Q_N		Q_{N+1}	J	K
0	→	0	0	X
0	→	1	1	X
1	→	0	X	1
1	→	1	X	0

Step 4: The Karnaugh maps for the J and K inputs of the flip-flops are shown in Figure 8–36. The UP/DOWN control input, Y , is considered one of the state variables along with Q_0 , Q_1 , and Q_2 . Using the next-state table, the information in the “Flip-Flop Inputs” column of Table 8–12 is transferred onto the maps as indicated for each present state of the counter.

PRESENT STATE			NEXT STATE					
			Y = 0 (DOWN)			Y = 1 (UP)		
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0	Q_2	Q_1	Q_0
0	0	0	1	0	0	0	0	1
0	0	1	0	0	0	0	1	1
0	1	1	0	0	1	0	1	0
0	1	0	0	1	1	1	1	0
1	1	0	0	1	0	1	1	1
1	1	1	1	1	0	1	0	1
1	0	1	1	1	1	1	0	0
1	0	0	1	0	1	0	0	0


Y = UP/DOWN control input.

      

Step 5: The 1s are combined in the largest possible groupings, with “don’t cares” (Xs) used where possible. The groups are factored, and the expressions for the J and K inputs are as follows:

$$\begin{aligned}
 J_0 &= Q_2 Q_1 Y + Q_2 \bar{Q}_1 \bar{Y} + \bar{Q}_2 \bar{Q}_1 Y + \bar{Q}_2 Q_1 \bar{Y} & K_0 &= \bar{Q}_2 \bar{Q}_1 \bar{Y} + \bar{Q}_2 Q_1 Y + Q_2 \bar{Q}_1 Y + Q_2 Q_1 \bar{Y} \\
 J_1 &= \bar{Q}_2 Q_0 Y + Q_2 Q_0 \bar{Y} & K_1 &= \bar{Q}_2 Q_0 \bar{Y} + Q_2 Q_0 Y \\
 J_2 &= Q_1 \bar{Q}_0 Y + \bar{Q}_1 \bar{Q}_0 \bar{Y} & K_2 &= Q_1 \bar{Q}_0 \bar{Y} + \bar{Q}_1 \bar{Q}_0 Y
 \end{aligned}$$

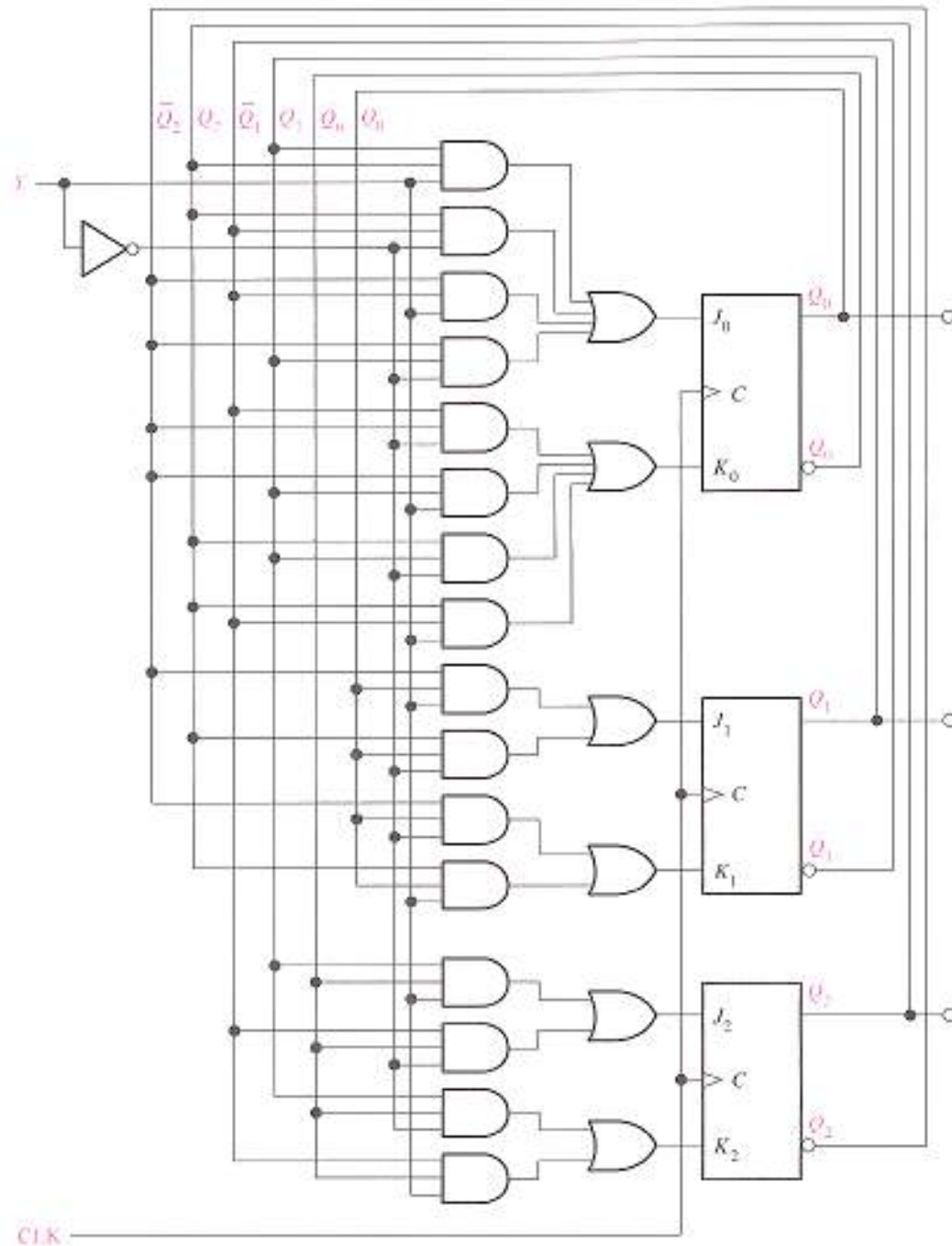Step 6: The J and K equations are implemented with combinational logic, and the complete counter is shown in Figure 8–37.



Reference:

- [1] Thomas L. Floyd, "Digital Fundamentals" 11th edition, Prentice Hall.
- [2] M. Morris Mano, "Digital Logic & Computer Design" Prentice Hall.
- [3] Mixed contents from Vahid And Howard.



Thanks

