



EEE 3101: Digital Logic and Circuits

Decoder & Encoder

Course Teacher: Nafiz Ahmed Chisty

Head, Department of EEE

Associate Professor, Department of EEE & CoE

Faculty of Engineering

Room# D0105, D Building

Email: chisty@aiub.edu


Website: <http://engg.aiub.edu/faculties/nafiz>

Website: www.nachisty.com



Decoder

 A **n -to- 2^n decoder** takes an **n -bit** input and produces 2^n outputs. The n inputs represent a binary number that determines which of the 2^n outputs is *uniquely* true.



Example:

- Reception counter: When you reach an Academic Institute
- Receptionist asks: Which Dept. to go?
- Based on your Specific answer, Receptionist redirects you to the specific building.

The job of the Decoder is to **Decode!**

-It knows what to do for a fixed question.

Use:

- Memory addressing
- Address to a particular location.


2-to-4 decoder

Truth table:


Input		Output			
S_1	S_0	Q_0	Q_1	Q_2	Q_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

For instance, if the input $S_1 S_0 = 10$ (decimal 2), then output Q_2 is **true**, and Q_0, Q_1, Q_3 are all **false**. This circuit “decodes” a binary number into a “one-of-four” code.

Block Diagram:

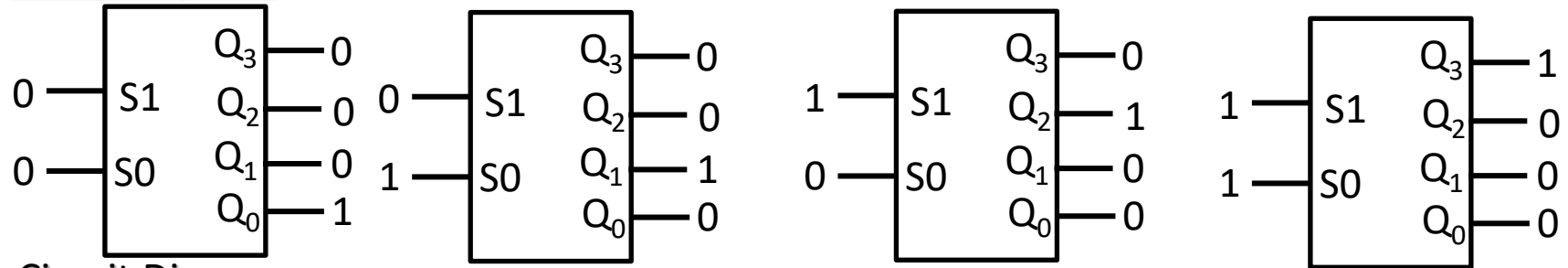

Circuit Diagram:

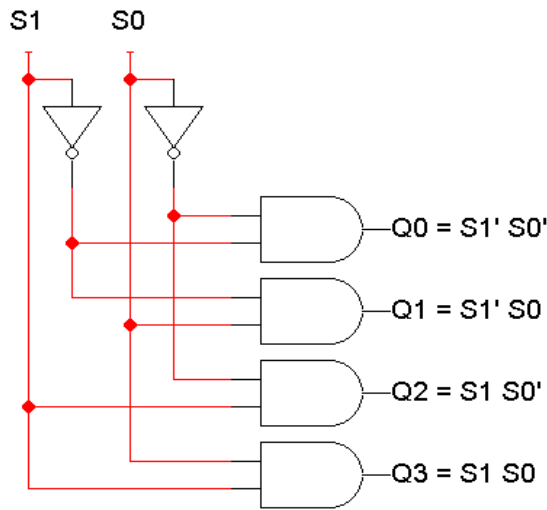

$$Q_0 = S_1' S_0'$$


$$Q_1 = S_1' S_0$$

$$Q_2 = S_1 S_0'$$

$$Q_3 = S_1 S_0$$

3-to-8 decoder


Block Diagram:

 


Truth table:

Input			Output							
S_2	S_1	S_0	Q_0	Q_1	Q_2	Q_3	Q_4	Q_5	Q_6	Q_7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

Circuit Diagram:

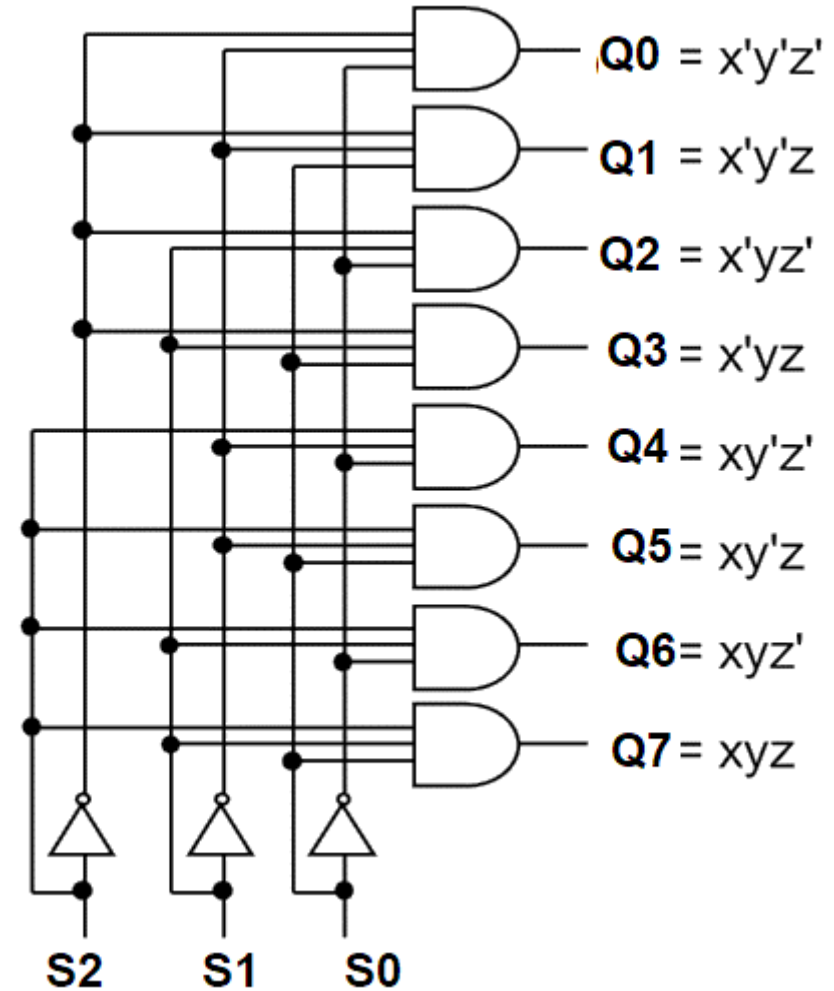


3-to-8 decoder (Active High Output)

 

Input			Output							
S_2	S_1	S_0	Q_0	Q_1	Q_2	Q_3	Q_4	Q_5	Q_5	Q_7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

3-to-8 decoder (Active Low Output)

 

Input			Output							
S_2	S_1	S_0	Q_0	Q_1	Q_2	Q_3	Q_4	Q_5	Q_5	Q_7
0	0	0	0	1	1	1	1	1	1	1
0	0	1	1	0	1	1	1	1	1	1
0	1	0	1	1	0	1	1	1	1	1
0	1	1	1	1	1	0	1	1	1	1
1	0	0	1	1	1	1	0	1	1	1
1	0	1	1	1	1	1	1	0	1	1
1	1	0	1	1	1	1	1	1	0	1
1	1	1	1	1	1	1	1	1	1	0

- Decoding ONLY a specific sequence:


The output is 1 only when:

$$A_0 = 1$$

$$A_1 = 0$$

$$A_2 = 0$$

$$A_3 = 1$$

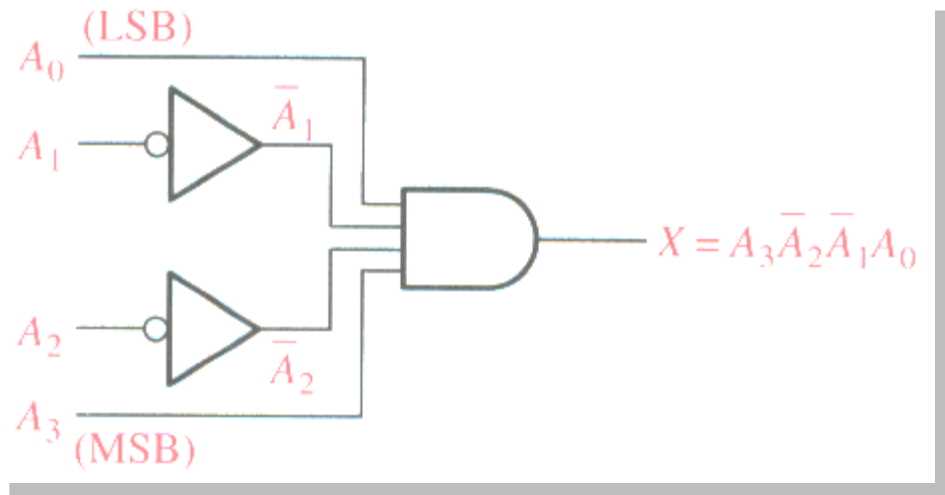


Use:

 - 1) Encryption system,
- 2) Counter decoding...etc.

Enable inputs

- Many devices have an additional **enable input**, which is used to “**activate**” or “**deactivate**” the device.



- For a decoder,
 - EN=0 “deactivates” the decoder. By convention, that means *all* of the decoder’s outputs are 0.
 - EN=1 activates the decoder, so it behaves as specified earlier. Exactly one of the outputs will be 1.

EN	S1	S0	Q0	Q1	Q2	Q3
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1



EN	S1	S0	Q0	Q1	Q2	Q3
0	x	x	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1


$$Q0 = S1' S0' EN$$

$$Q1 = S1' S0 EN$$


$$Q2 = S1 S0' EN$$

$$Q3 = S1 S0 EN$$

2-to-4

 

3-to-8

 



Implementing Functions using Decoders

Design example: addition

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


$$C(X,Y,Z) = \Sigma (3,5,6,7)$$

$$S(X,Y,Z) = \Sigma (1,2,4,7)$$

  

Decoder expansion

 - Combine two or more small decoders with **enable** inputs to form a larger decoder.
- Here a 3-to-8 decoder has been constructed from **two** 2-to-4 decoders:



S2	S1	S0	Q0	Q1	Q2	Q3	Q4	Q5	Q6	Q7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

EN	S1	S0	Q0	Q1	Q2	Q3
0	x	x	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

Use two 3 to 8 decoders to make 4 to 16 decoder



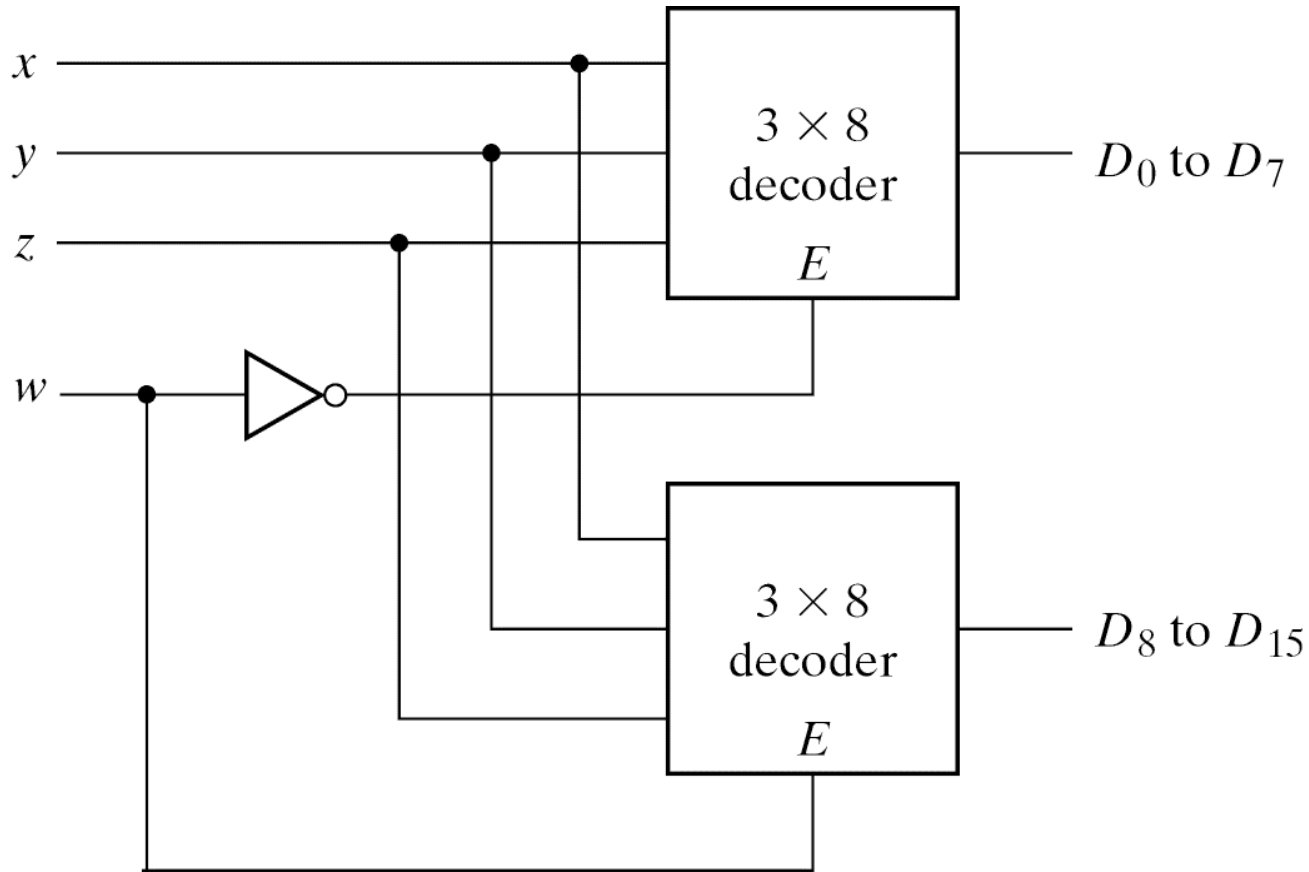


Fig. 4-20 4 × 16 Decoder Constructed with Two 3 × 8 Decoders

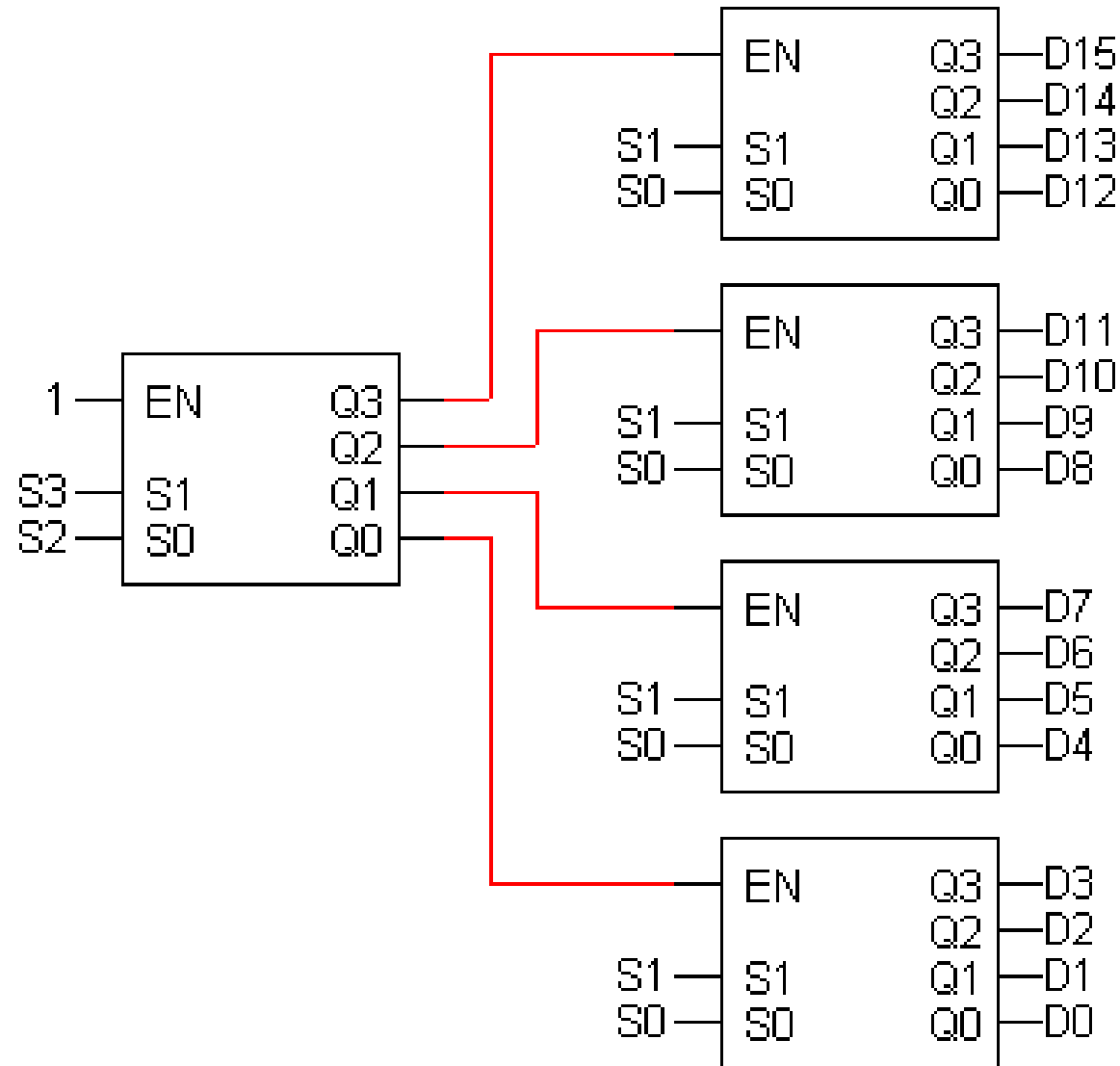4-to-16 decoder using only 2-to-4 decoders (no gates)



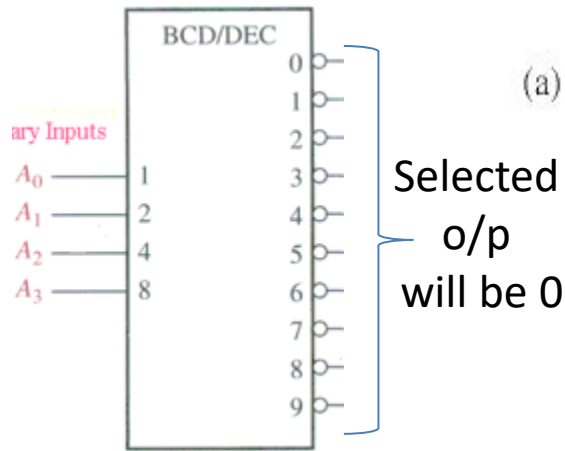
BCD-to-decimal decoder (Active Low Output)




DECIMAL DIGIT	BCD CODE			
	A_3	A_2	A_1	A_0
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1

Decimal outputs




(b)

 


BCD-to-7-segement decoder

 

DECIMAL DIGIT	INPUTS				SEGMENT OUTPUTS						
	D	C	B	A	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	1	0	1	1
10	1	0	1	0	X	X	X	X	X	X	X
11	1	0	1	1	X	X	X	X	X	X	X
12	1	1	0	0	X	X	X	X	X	X	X
13	1	1	0	1	X	X	X	X	X	X	X
14	1	1	1	0	X	X	X	X	X	X	X
15	1	1	1	1	X	X	X	X	X	X	X

   

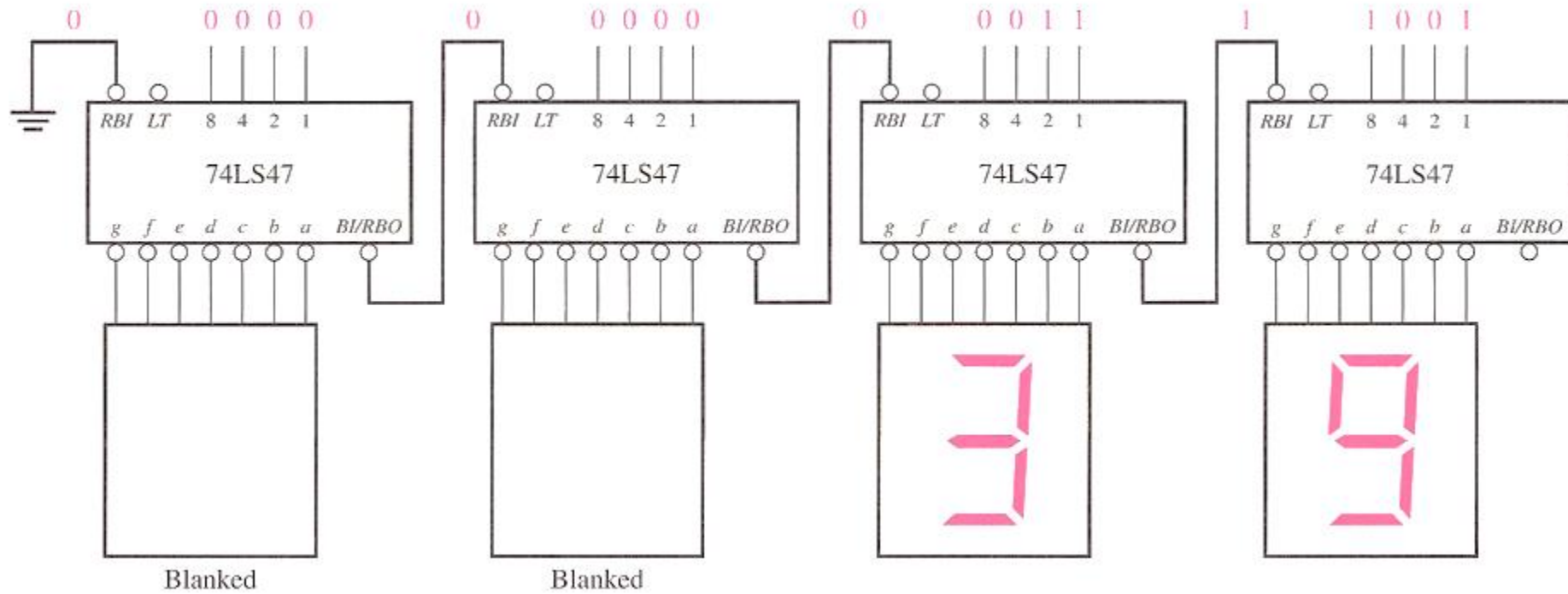


Encoders

An **Encoder** is a combinational logic circuit that performs a “**reverse**” decoder function.

An Encoder accepts an active level on one of its inputs representing a digit, such as a decimal or octal digit, and converts it to a coded output, such as BCD or binary.

Encoders can also be devised to encode various symbols and alphabetic characters. The process of converting from familiar symbols or numbers to a coded format is called **Encoding**.



2ⁿ-to-n Encoder:

 

8-to-3 Binary Encoder

At any one time, only one input line has a value of 1.

Inputs								Outputs		
I_0	I_1	I_2	I_3	I_4	I_5	I_6	I_7	y_2	y_1	y_0
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

 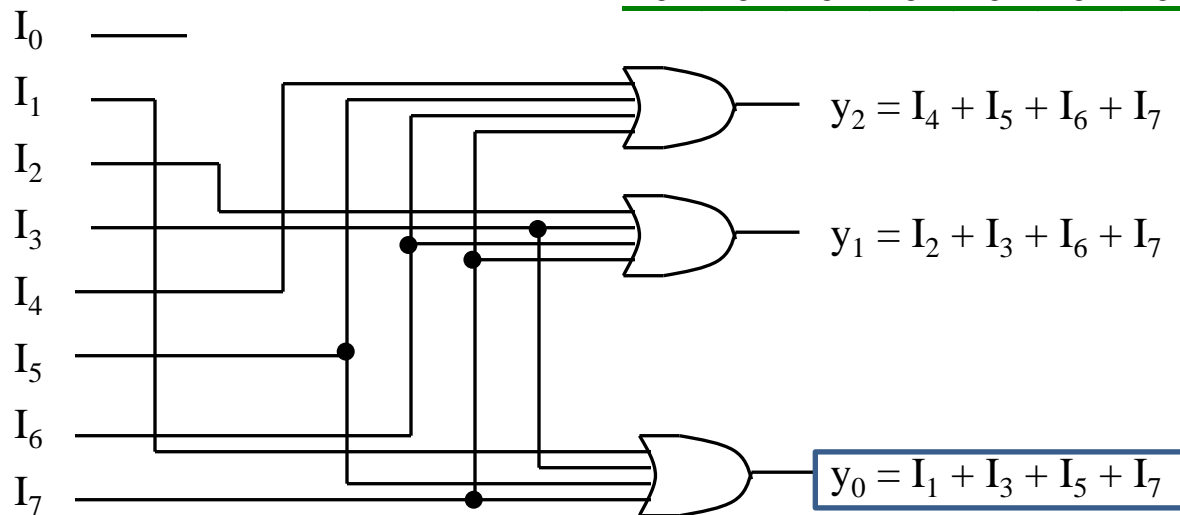

8-to-3 Priority Encoder

- What if more than one input line has a value of 1?

Example:

- For the above mentioned problem, let's give priority to higher bits
- Ignore "lower priority" inputs.
- The sequence is:

$$7 > 6 > 5 > 4 > 3 > 2 > 1 > 0$$

- Idle** indicates that no input is a 1.

Inputs								Outputs			Idle
I ₀	I ₁	I ₂	I ₃	I ₄	I ₅	I ₆	I ₇	Y ₂	Y ₁	Y ₀	
0	0	0	0	0	0	0	0	x	x	x	1
1	0	0	0	0	0	0	0	0	0	0	0
X	1	0	0	0	0	0	0	0	0	1	0
X	X	1	0	0	0	0	0	0	1	0	0
X	X	X	1	0	0	0	0	0	1	1	0
X	X	X	X	1	0	0	0	1	0	0	0
X	X	X	X	X	1	0	0	1	0	1	0
X	X	X	X	X	X	1	0	1	1	0	0
X	X	X	X	X	X	X	1	1	1	1	0

Priority Encoder (8 to 3 encoder)

- Assign priorities to the inputs
- When more than one inputs are asserted, the output generates the code of the input with the highest priority: $7 > 6 > 5 > 4 > 3 > 2 > 1 > 0$

Priority Encoder :

$H7 = I7$ (Highest Priority)

$H6 = I6 \cdot I7'$

$H5 = I5 \cdot I6' \cdot I7'$

$H4 = I4 \cdot I5' \cdot I6' \cdot I7'$

$H3 = I3 \cdot I4' \cdot I5' \cdot I6' \cdot I7'$

$H2 = I2 \cdot I3' \cdot I4' \cdot I5' \cdot I6' \cdot I7'$

$H1 = I1 \cdot I2' \cdot I3' \cdot I4' \cdot I5' \cdot I6' \cdot I7'$

$H0 = I0 \cdot I1' \cdot I2' \cdot I3' \cdot I4' \cdot I5' \cdot I6' \cdot I7'$


$IDLE = I0' \cdot I1' \cdot I2' \cdot I3' \cdot I4' \cdot I5' \cdot I6' \cdot I7'$

Encoder

$Y0 = I1 + I3 + I5 + I7$

$Y1 = I2 + I3 + I6 + I7$

$Y2 = I4 + I5 + I6 + I7$

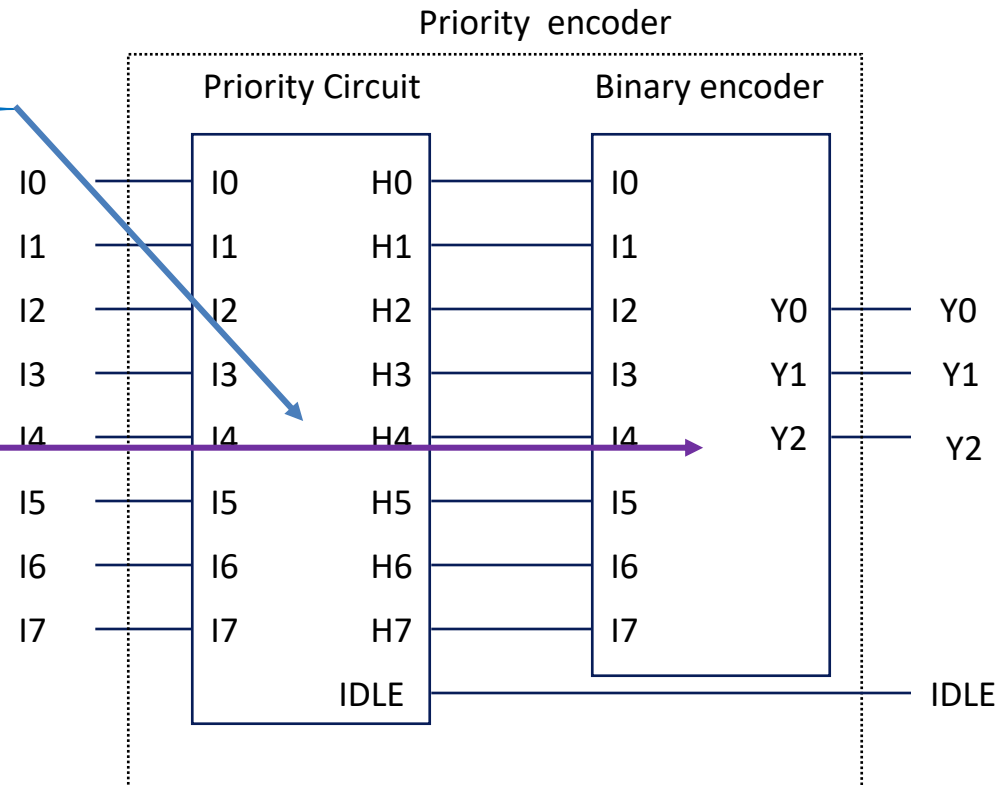

The Decimal to - BCD Priority Encoder:

Let Priority is given to the higher order digits. Requirements to activate A_0 :

1) A_0 is HIGH if 1 is HIGH and 2,4,6,8 LOW

A_0 is HIGH if 3 is HIGH and 4,6,8 LOW

A_0 is HIGH if 5 is HIGH and 6,8 LOW

A_0 is HIGH if 7 is HIGH and 8 LOW

A_0 is HIGH if 9 is HIGH

$$\text{Therefore, } A_0 = 1.2'.4'.6'.8' + 3.4'.6'.8' + 5.6'.8' + 7.8' + 9$$

2) A_1 is HIGH if 2 is HIGH and 4,5,8,9 LOW

A_1 is HIGH if 3 is HIGH and 4,5,8,9 LOW

A_1 is HIGH if 6 is HIGH and 8,9 LOW

A_1 is HIGH if 7 is HIGH and 8,9 LOW

$$\text{Therefore, } A_1 = (2+3)4'.5'.8'.9' + (6+7)8'.9'$$

3) A_2 is HIGH if 4 is HIGH and 8,9 LOW

A_2 is HIGH if 5 is HIGH and 8,9 LOW




A_2 is HIGH if 6 is HIGH and 8,9 LOW

A_2 is HIGH if 7 is HIGH and 8,9 LOW

$$\text{Therefore, } A_2 = (4+5+6+7)8'.9'$$

4) A_3 is HIGH if 8 & 9 are HIGH

$$\text{Therefore, } A_3 = 8.9$$

   



Reference:

- [1] Thomas L. Floyd, "Digital Fundamentals" 11th edition, Prentice Hall.
- [2] M. Morris Mano, "Digital Logic & Computer Design" Prentice Hall.
- [3] Mixed contents from Vahid And Howard.





Thanks

