

NAME: ANKON SARKER LINKON

ID:19-40895-2

SEC:B

Ankon Sarker Linkon

19-40895-2

①

Only 4 people are allowed in a queue with maintaining 3 feet distance in front of a small room in this vaccination center. Since each applicant has a digital taken with a sensor, the 4 applicants upon entering the room would each set off an input of high, when anyone stay behind, the sensor would give off a low input for them (0) and when more than 2 inputs are detected to be high (1), the alarm would go off which would be represented by (1) high. If there are 4 people $2^4 = 16$ different possibilities can exist which will be outlined by a table below from the table, we will draw a k-map and find the sop expression and illustrated the system by cmos logic.

For 4 people, We consider A, B, C, D.

NO	A	B	C	D	Y
0	0	0	0	0	0
1	0	0	0	1	0
2	0	0	1	0	0
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	0
6	0	1	1	0	0
7	0	1	1	1	1
8	1	0	0	0	0
9	1	0	0	1	0
10	1	0	1	0	0
11	1	0	1	1	1
12	1	1	0	0	0
13	1	1	0	1	1
14	1	1	1	0	1
15	1	1	1	1	1

Ankon Sarkar Linkon

19-40895-2

(2)

AB \ CD	00	01	10	11
00	0	0	0	0
01	0	0	1	0
10	0	1	1	1
11	0	0	1	0

Now grouping.

$$(13, 15) = ABD$$

$$(15, 11) = ACD$$

$$(7, 15) = BCD$$

$$(15, 14) = ABC$$


$$\text{SOP form} = ABD + BCD + ACD + ABC$$

Anken Sarker Linken

19-90895-2

③
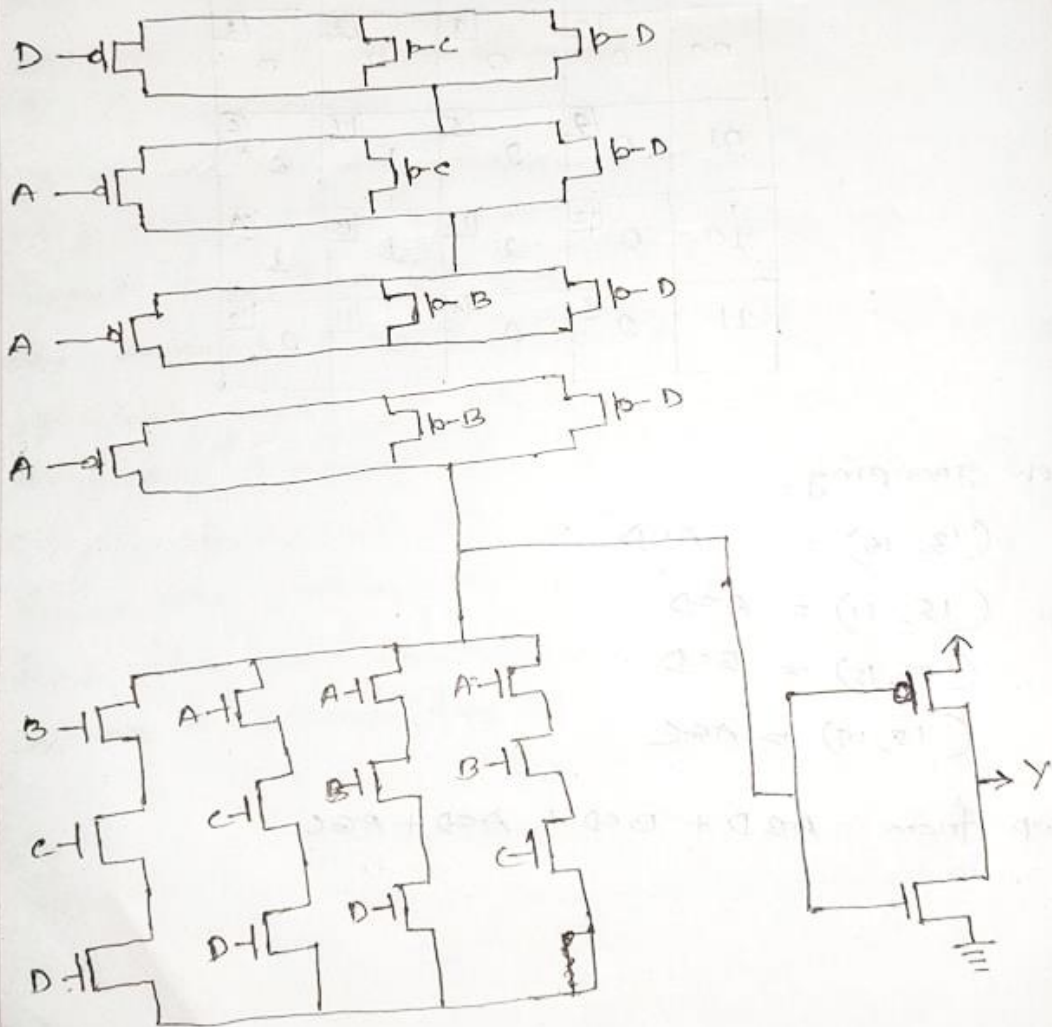
$$Y = \overline{BCD} + \overline{ACD} + \overline{ABD} + \overline{ABC}$$



Ankon Sarker Linkon

19-10895-2

④

Ans to the Ques no(ii)

given, $M = C + O + V + I + D$

$$\therefore C = 4, O = 80, V = 8, I = 9, D = 5$$

$$M = 4 + 0 + 8 + 9 + 5$$

$$= 26$$

and also given

$$\text{duty cycle} = N\%$$

$$\text{and } N = 100 - M$$

$$= 100 - 26$$

$$= 74$$

$$\therefore \text{duty cycle } N = 74\%$$

$$M_5 = 235 \text{ Hz} > 250 \text{ Hz}$$

$$235 \text{ Hz} \Rightarrow < 250 \text{ Hz} \text{ therefore}$$

$$\text{frequency, } F = 400 \text{ Hz}$$

$$N = 74\%$$

$$C = 50 \mu F$$



SHOT ON POCO X3

Arkon Sarker Linkon

S 2580P - 01

19-90895-2

⑤

We know that

$$T = \frac{1}{f}$$
$$= \frac{1}{400} = 0.0025$$

∴ Time high and time low -

$$T_H = 0.74 \times 0.0025 = 1.85 \text{ ms}$$

$$T_L = 0.26 \times 0.0025 = 0.65 \text{ ms}$$

$$\therefore T_H = 1.85 \text{ ms}, T_L = 0.65 \text{ ms}$$

Ankon Sankar Linkon

19-40895-2

⑥

Value of R_2 :

$$T_L = 0.693 R_2 C$$

$$\begin{aligned}\Rightarrow R_2 &= \frac{T_L}{0.693 \times C} \\ &= \frac{0.65 \times 10^{-3}}{(0.693 \times 50 \times 10^{-6})} \\ &= 18.76 \Omega\end{aligned}$$

Value of R_1 .

$$T_H = 0.693 (R_1 + R_2) C$$

$$\begin{aligned}\Rightarrow (R_1 + R_2) &= \frac{T_H}{0.693 \times C} \\ \Rightarrow (R_1 + R_2) &= \frac{1.85 \times 10^{-3}}{0.693 \times 50 \times 10^{-6}}\end{aligned}$$

$$\begin{aligned}\Rightarrow R_1 &= (53.39 - 18.76) \Omega \\ &= 34.63 \Omega\end{aligned}$$

